

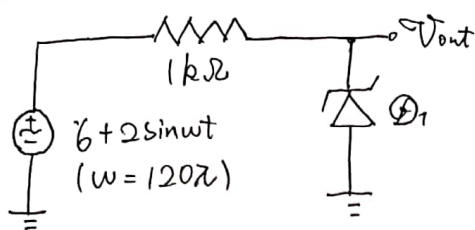


### Problem #1 (diode circuit)

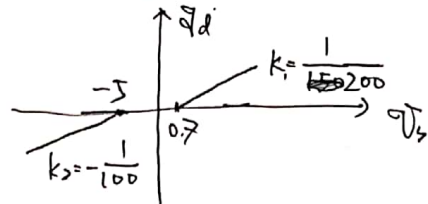

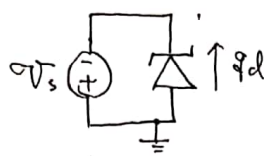The  $i$ - $v$  curve of the diode circuit  $D_1$




Plot the diagram of  $V_{out}$ .

$$R_L = 100 \quad V_{out} = \begin{cases} 0 & V_{in} \in [-5, 4] \\ \frac{6 + 2 \sin \omega t - 0.7}{1100} \times 100 + 5 & V_{in} \in [5, 8] \end{cases}$$

$$R_{on} = 200, R_z = 100$$

$$V_{in} \in [-5, 4]$$

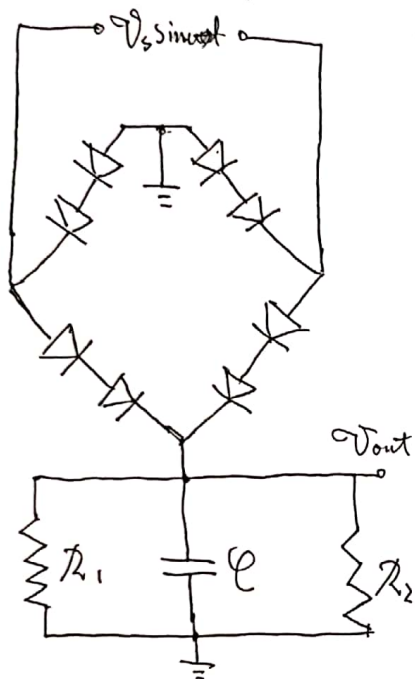Prob. #2. (Rectifier): Suppose the turn-on voltage of all the diodes are  $V_{on}$  and there are no inner resistance in them. Find



(1)  $I_{dc}$  (2)  $P_{av}$ . (suppose  $R_1, R_2 \ll C \gg T$ ).


(3) Discuss could the circuit work if the inner resistance of diodes are comparable with  $R_1$  or  $R_2$  (Just a thinking problem and do not require in exam)

$$I (I_{dc} = \frac{V_s - 4V_{on}}{R_1 \parallel R_2}; P_{av} = V_s - 2V_{on})$$

II. It will not work since the  $V_{out}$  is too small)

Reason:  $R_{load} \ll R_{on}$

### Prob #3 (Rectifier)

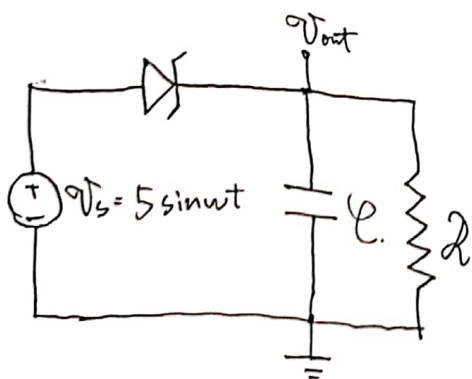

For the diode in the circuit,  $V_{on} = 0.7V$  and  $V_z = 5V$ .

Plot the curve of  $V_{out}$  and  $V_{on}$  in the same graph.



( $R \cdot C \gg T$ ,  $T$  is the period of  $v_s$ )

Mention that you need to show the relationship between  $V_{out}$  and  $V_{on}$  when you plot the diagram.


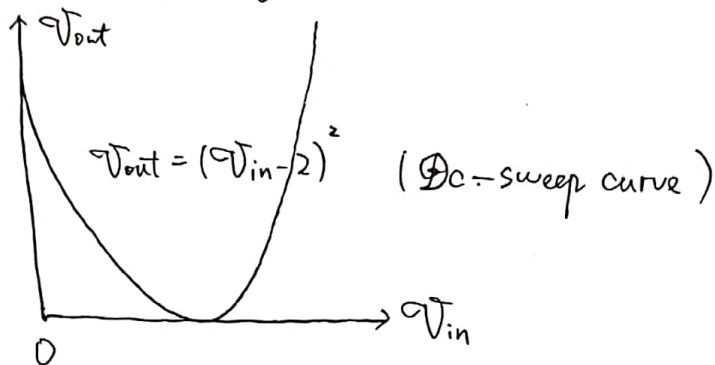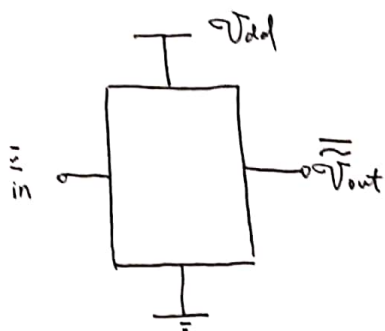
# Prob #4 (General Amplifier)


For the following Amplifier, find  $V_{out}$ .



(1)  $V_{in} = 1 + 0.1 \sin(120\pi t)$

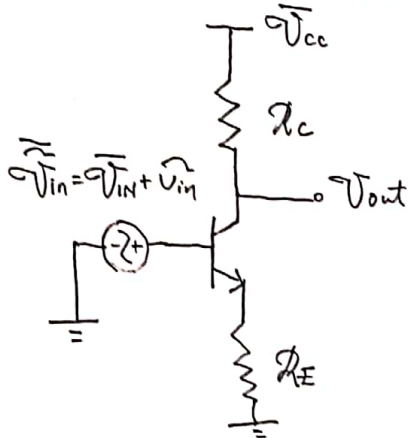(2) Discuss at which point, it's ~~hardest~~ the most difficult to approximate the amplifier into a small-signal model if the DC input voltage  $\bar{V}_{in}$  remains a constant. (I.  $\bar{V}_{in} = 1$  II.  $\bar{V}_{in} = 2$  III.  $\bar{V}_{in} = 3$ )

Prob #5 : For the following circuit,  $I_s = 1 \times 10^{-16}$ ,  $\beta = 100$ ,  $V_A = 100$ .




(1). Suppose  $\bar{V}_{in} = 0.7V$ ,  $\bar{V}_{cc} = 3V$ ,  $R_c = R_E = 5000\Omega$   
Find the value of  $g_m$ ,  $r_o$ ,  $r_\pi$

(Hint: Suppose the node voltage  $\bar{v}_E$  is  $\bar{V}_E$ ).


(2) Calculate the small signal gain  $A_v = \frac{v_{out}}{v_{in}}$   
(You do not need to find the value, only need to derive the expression with  $g_m$ ,  $r_\pi$ ,  $r_o$ ).

Prob #6 : Suppose ( $\beta \neq \infty$  &  $V_A \neq \infty$ ), Find  $A_v$  using  $r_\pi$ ,  $r_o$  &  $g_m$ .

(Suppose  $\omega$  is high)

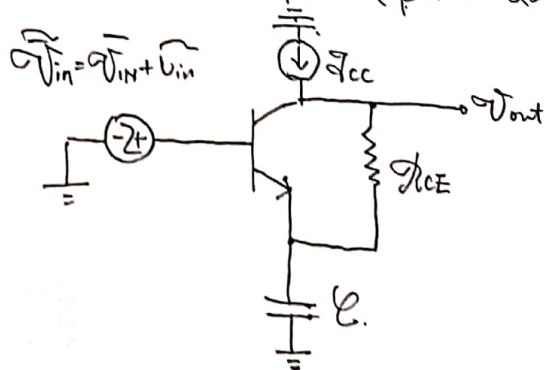


Prob # 3

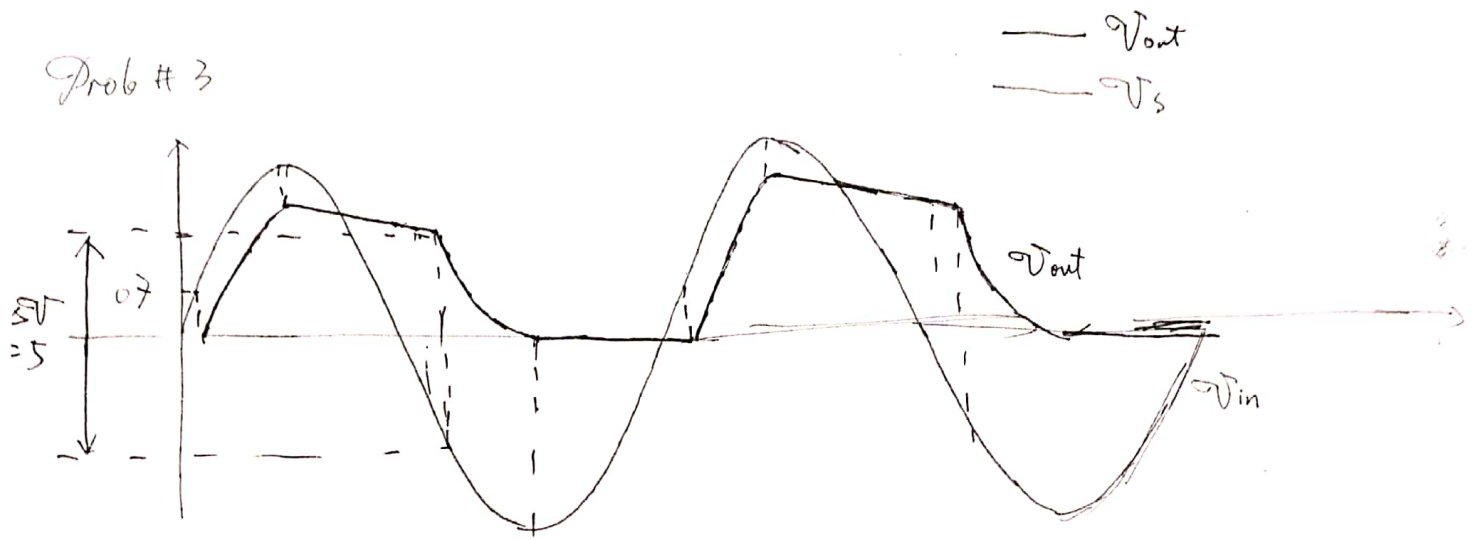

Prob # 4 (1)  $V_s = 1 - 0.2 \sin 120 \pi t$   
 (2)  $V_{in} = 2$  is the most difficult.

Prob # 5.


(1) Suppose  $\bar{V}_E$ , then we have

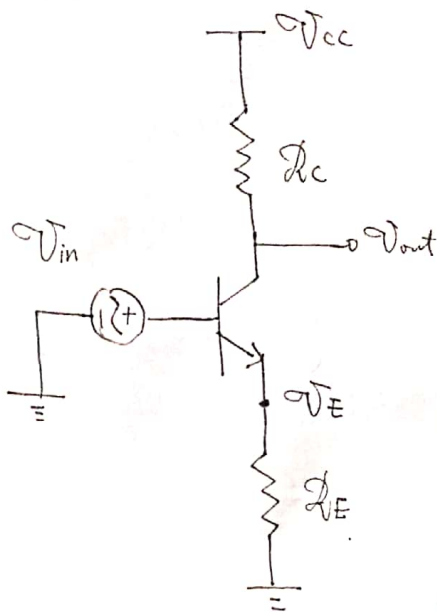

$$\begin{aligned} \bar{V}_{cc} - \bar{V}_{out} &= I_c \cdot R_c \\ \bar{V}_E - 0 &= I_E \cdot R_E \\ I_c &= I_s \left[ \exp\left(\frac{q(\bar{V}_{in} - \bar{V}_E)}{kT}\right) - 1 \right] \left( 1 + \frac{\bar{V}_{out} - \bar{V}_E}{V_{AF}} \right) \\ I_E &= I_B + I_{BC} \\ I_c &= \beta \cdot I_B \end{aligned}$$

$\Rightarrow$  Solution

(2) Small signal model:

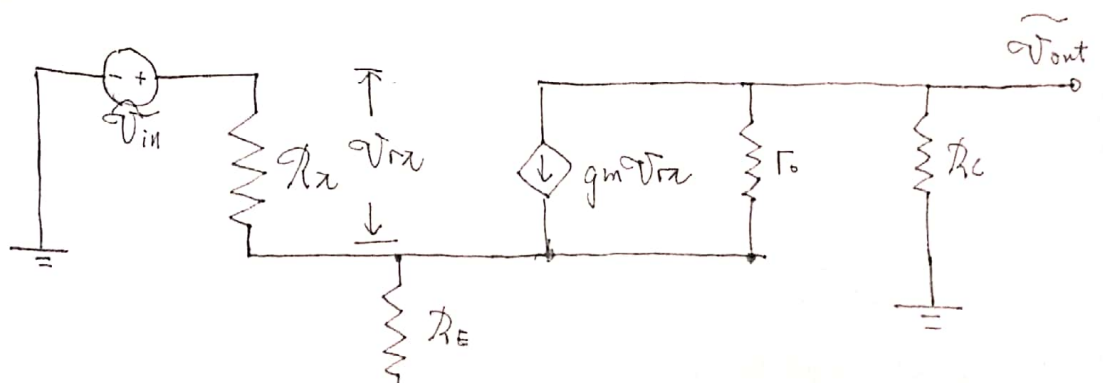

扫描全能王 创建

Prob #6. Small signal model:

