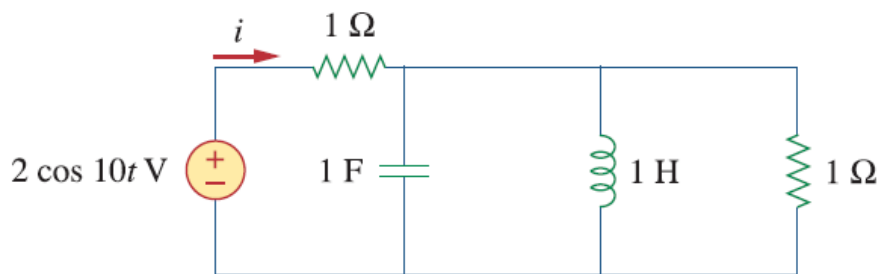



**10.1** Determine  $i$  in the circuit of Fig. 10.50.



**Figure 10.50**

For Prob. 10.1.


**10.25** Solve for  $i_o$  in Fig. 10.73 using mesh analysis.

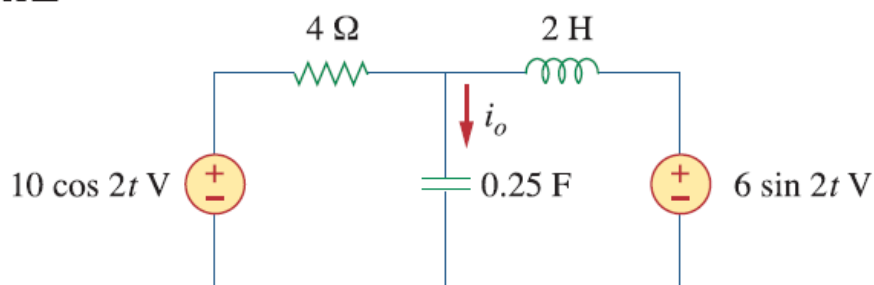

**Figure 10.73**

For Prob. 10.25.


**10.49** Using source transformation, find  $i$  in the circuit of Fig. 10.94.

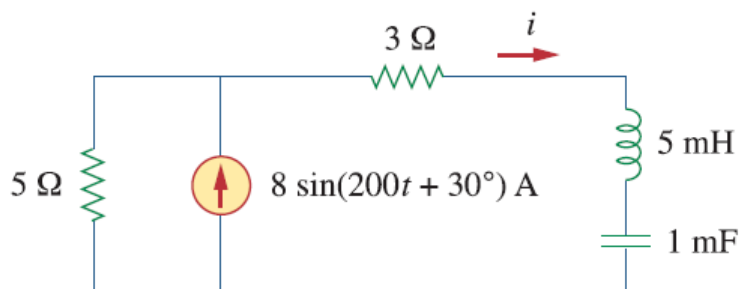

**Figure 10.94**

For Prob. 10.49.


**10.58** For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals  $a$ - $b$ .

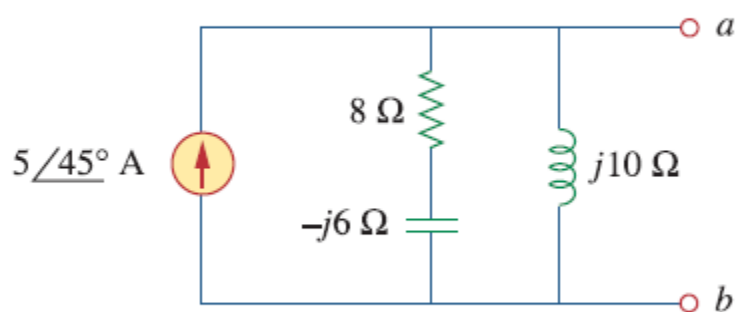

**Figure 10.101**

For Prob. 10.58.

**10.79** For the op amp circuit in Fig. 10.122, obtain  $v_o(t)$ .

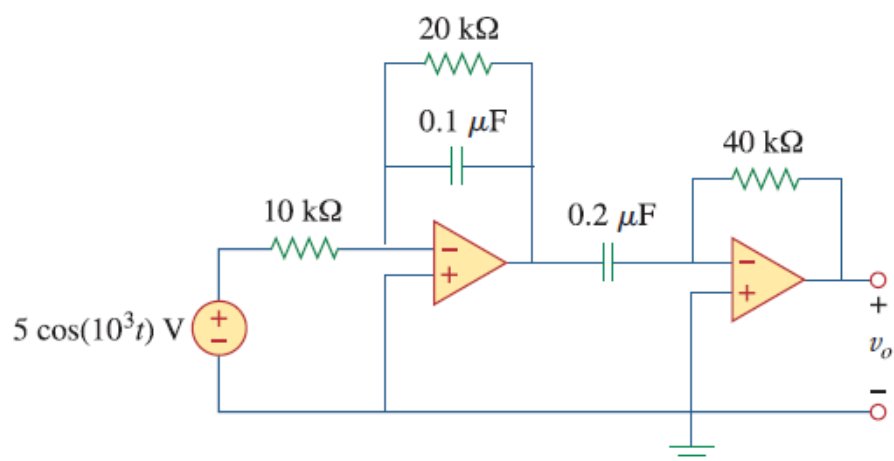

**Figure 10.122**


For Prob. 10.79.

**10.89** The op amp circuit in Fig. 10.131 is called an *inductance simulator*. Show that the input impedance is given by

$$Z_{\text{in}} = \frac{V_{\text{in}}}{I_{\text{in}}} = j\omega L_{\text{eq}}$$

where

$$L_{\text{eq}} = \frac{R_1 R_3 R_4}{R_2} C$$

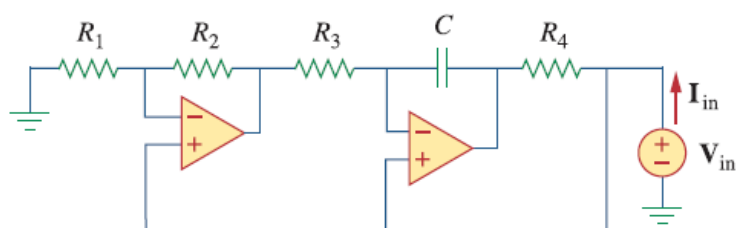


**Figure 10.131**

For Prob. 10.89.

**10.92** The oscillator circuit in Fig. 10.134 uses an ideal op amp.

- Calculate the minimum value of  $R_o$  that will cause oscillation to occur.
- Find the frequency of oscillation.

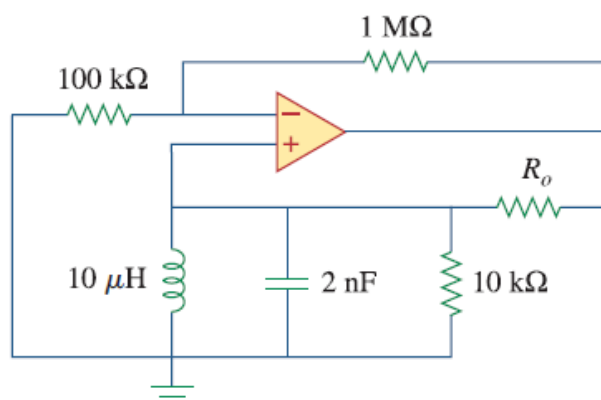

**Figure 10.134**

For Prob. 10.92.