


- 13.3** Two coils connected in series-aiding fashion have a total inductance of 500 mH. When connected in a series-opposing configuration, the coils have a total inductance of 300 mH. If the inductance of one coil ( $L_1$ ) is three times the other, find  $L_1$ ,  $L_2$ , and  $M$ . What is the coupling coefficient?

**13.24** In the circuit of Fig. 13.93,



**ML**


- find the coupling coefficient,
- calculate  $v_o$ ,
- determine the energy stored in the coupled inductors at  $t = 2$  s.

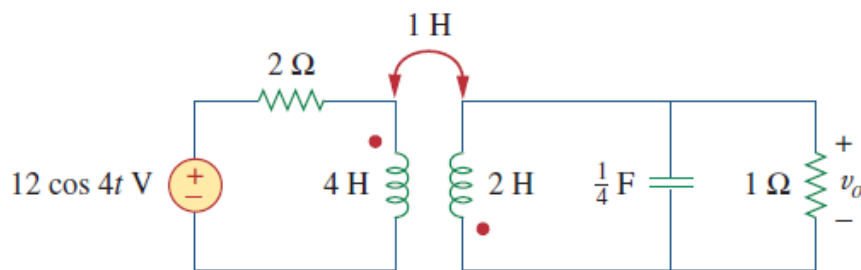

**Figure 13.93**

For Prob. 13.24.


- 13.29** In the circuit of Fig. 13.98, find the value of the coupling coefficient  $k$  that will make the 10- $\Omega$  resistor dissipate 320 W. For this value of  $k$ , find the energy stored in the coupled coils at  $t = 1.5$  s.

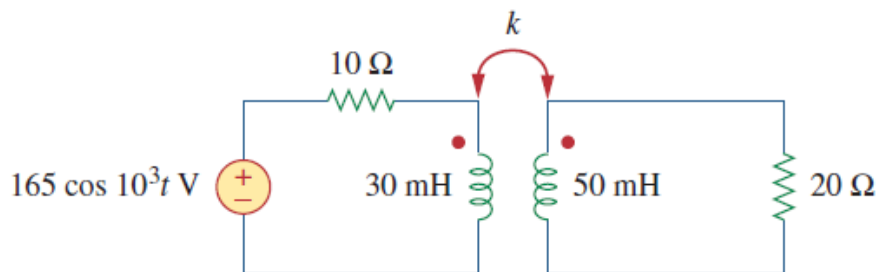

**Figure 13.98**

For Prob. 13.29.

13.41 Determine  $I_1$  and  $I_2$  in the circuit of Fig. 13.106.

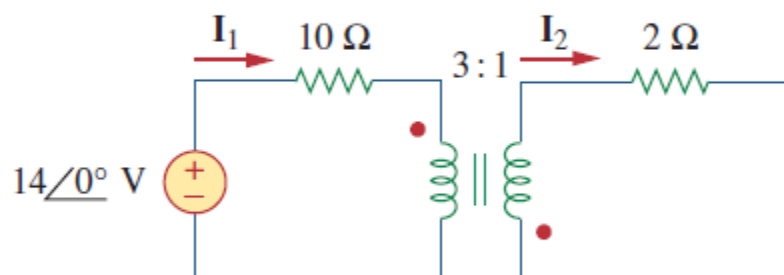


**Figure 13.106**

For Prob. 13.41.

13.53 Refer to the network in Fig. 13.118.



- Find  $n$  for maximum power supplied to the  $200\text{-}\Omega$  load.
- Determine the power in the  $200\text{-}\Omega$  load if  $n = 10$ .

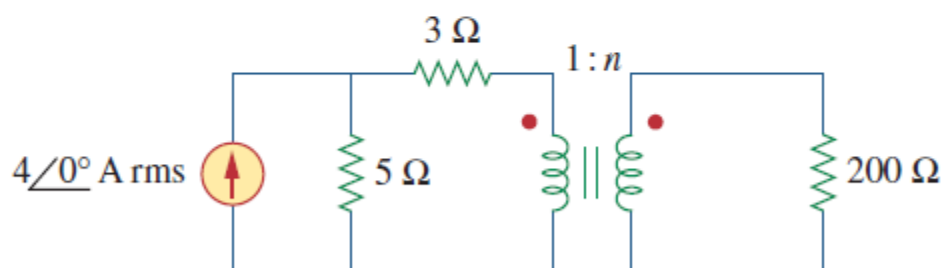


**Figure 13.118**

For Prob. 13.53.

**13.71** In the autotransformer circuit in Fig. 13.134, show that

$$Z_{\text{in}} = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L$$

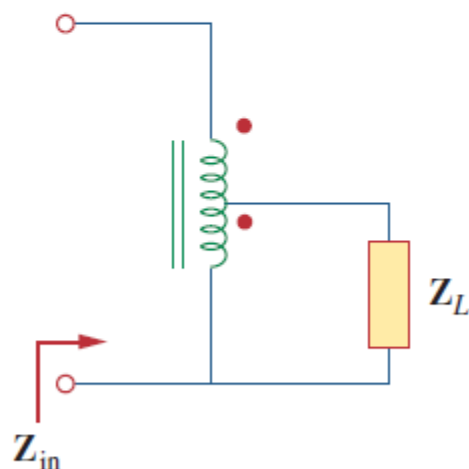

**Figure 13.134**

For Prob. 13.71.

**13.90** A 4-kVA, 2,400/240-V rms transformer has 250 turns on the primary side. Calculate:

- (a) the turns ratio,
- (b) the number of turns on the secondary side,
- (c) the primary and secondary currents.