



2. [BJT Forward-Active I-V Characteristics] For a npn BJT circuit as below:

- (a) [20%] When  $V_{BE} = 0.7 \text{ V}$  and  $V_{CE} = 2 \text{ V}$ , use proper equations provided in the course slides and the spice model above to calculate the transconductance gain ( $g_m$ ) and the output impedance ( $r_o$ ).
- (b) [15%] In Pspice, when  $V_{CE} = 2 \text{ V}$ , plot  $I_C$  versus  $V_{BE}$  (from 0 to 1 V). Find out the slope at  $V_{BE} = 0.7 \text{ V}$  and compare it with the  $g_m$  value calculated in (a).
- (c) [15%] In Pspice, when  $V_{BE} = 0.7 \text{ V}$ , plot  $I_C$  versus  $V_{CE}$  (from 0 to 5 V). Find out the inverse of slope at  $V_{CE} = 2 \text{ V}$  and compare it with the  $r_o$  value calculated in (a).



