

Topic 16

Programmable Logic Device

Outline


- Programmable Logic Devices (PLD)
- Programmable Logic Array (PLA)
- Programmable Array Logic (PAL)
- Complex Programmable Logic Device (CPLD)
- Field Programmable Gate Array (FPGA)

Programmable Logic Devices

- PLD
 - First introduced in 1970s
 - Can be viewed as a “black box” containing logic gates and programmable switches
 - The logic gates and programmable switches can be customized to implement specific logic circuit
 - Simple programmable logic devices (SPLD)
 - Programmable logic array (PLA)
 - Programmable array logic (PAL)
 - Complex programmable logic array (CPLD)
 - Field-programmable gate array (FPGA)


Programmable Logic Array (PLA)

 - Comprises a collection of buffers, inverters, AND gates, OR gates
- Can be used to realize logic circuit in sum-of-products (SOP) form,
- Example:
$$f = x'yz + xy'z'$$




Programmable Logic Array (PLA)

 - Buffers and inverters provide both true value and complement of each input
- AND plane provides the product terms
- OR plane provides the sum of the product terms
- Example:
 - $P1 = x1x2$
 - $P2 = x1x3'$
 - $P3 = x1'x2'x3$
 - $P4 = x1x3$
 - $F1 = P1 + P2 + P3$
 - $F2 = P1 + P3 + P4$



Programmable Logic Array (PLA)

 
- Each AND gate has $2 \times N$ inputs
 - N , number of primary inputs
- Each OR gate has M inputs
 - M , number of and gates
- **Problem:** size of the inputs
- Commercially available PLAs typically have:
 - 16 inputs
 - 32 AND gates
 - 8 OR gates
- Connections replaced by single lines, “x” indicates a connected input to the gate



Programmable Array Logic (PAL)


- Drawbacks of PLA
 - Hard to fabricate correctly due to the programmable connections
 - Special implementation of the programmable connections reduce the speed of circuits in PLA
- Solution: fix the OR plane – PAL
 - Less expensive
 - Better performance
 - Became popular in practical applications

Programmable Array Logic (PAL)

 


Programmable Array Logic (PAL)

 - In order to provide additional flexibility, an extra circuit is inserted between the OR output and the chip pin - *Macrocell*



PAL Example

 
- Compensate for the reduced flexibility
 - Various numbers of inputs to the OR gates




Complex Programmable Logic Devices (CPLD)

- Composed of multiple PAL/PLA-like circuit blocks
 - Blocks are connected through a set of interconnection wires
 - Blocks are connected to the IC chip pins through a set of I/O blocks
 - Number of blocks may vary from 2 to over 100
- Provides more inputs and outputs
- Provides more flexibility
- May accommodate bigger size circuit

CPLD

 

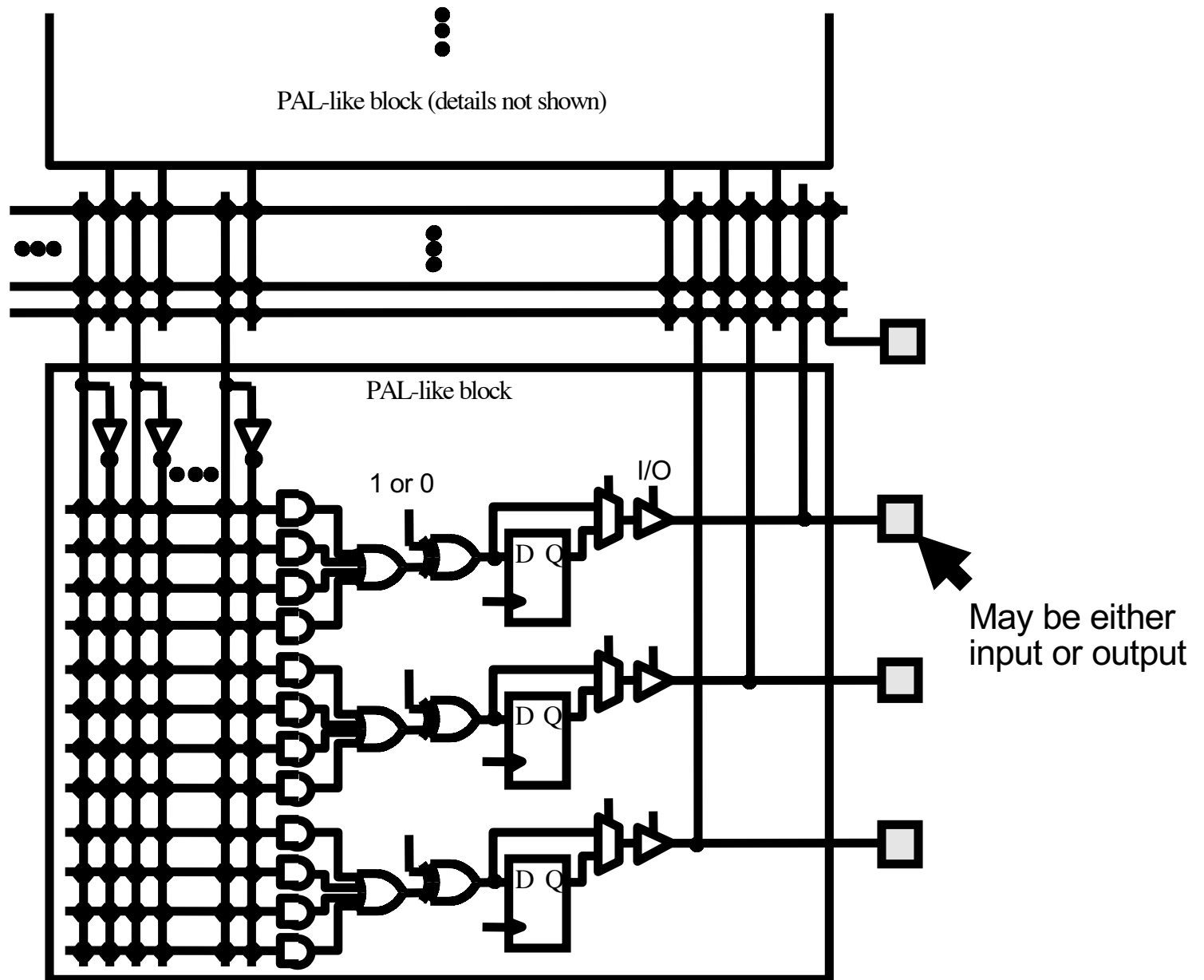

Field Programmable Gate Array (FPGA)

- First introduced by Xilinx in 1985
- Most FPGA providers are "fabless", allows
 - focus on device capability
 - improvement of design software
 - offering IP cores

Types of FPGA

- Reprogrammable
 - SRAM-based FPGA
 - Volatile, often the best choice for prototyping and development
 - Supports in-system-programming (ISP)
 - What we used in the labs
 - EEPROM-based (Flash-based) FPGA
- One-Time Programmable (OTP)
 - Anti-Fuse-based FPGA
 - EPROM-based FPGA

Configuration Technologies FPGA


- **Configure SRAM-based FPGA**
 - ISP, fast reconfiguration, but volatile
 - External device (EEPROM, may be onboard), programming on power up
- **Configure flash-based FPGA**
 - Similar to EEPROM programming devices
 - nonvolatile, may or may not support ISP
- **Configure EPROM-based FPGA**
 - Similar to EPROM programming devices
 - nonvolatile, off-board one-time configuration
- **Configure Anti-Fuse-based FPGA**
 - Fuse burning devices (electronically or optically)
 - nonvolatile, off-board one-time configuration

Internal Structure

- Composed of logic blocks and wires
 - Configurable Logic blocks (CLB)
 - I/O blocks (IOB)
 - Interconnection wires and switches


FPGA Architecture

- Typical FPGA architecture

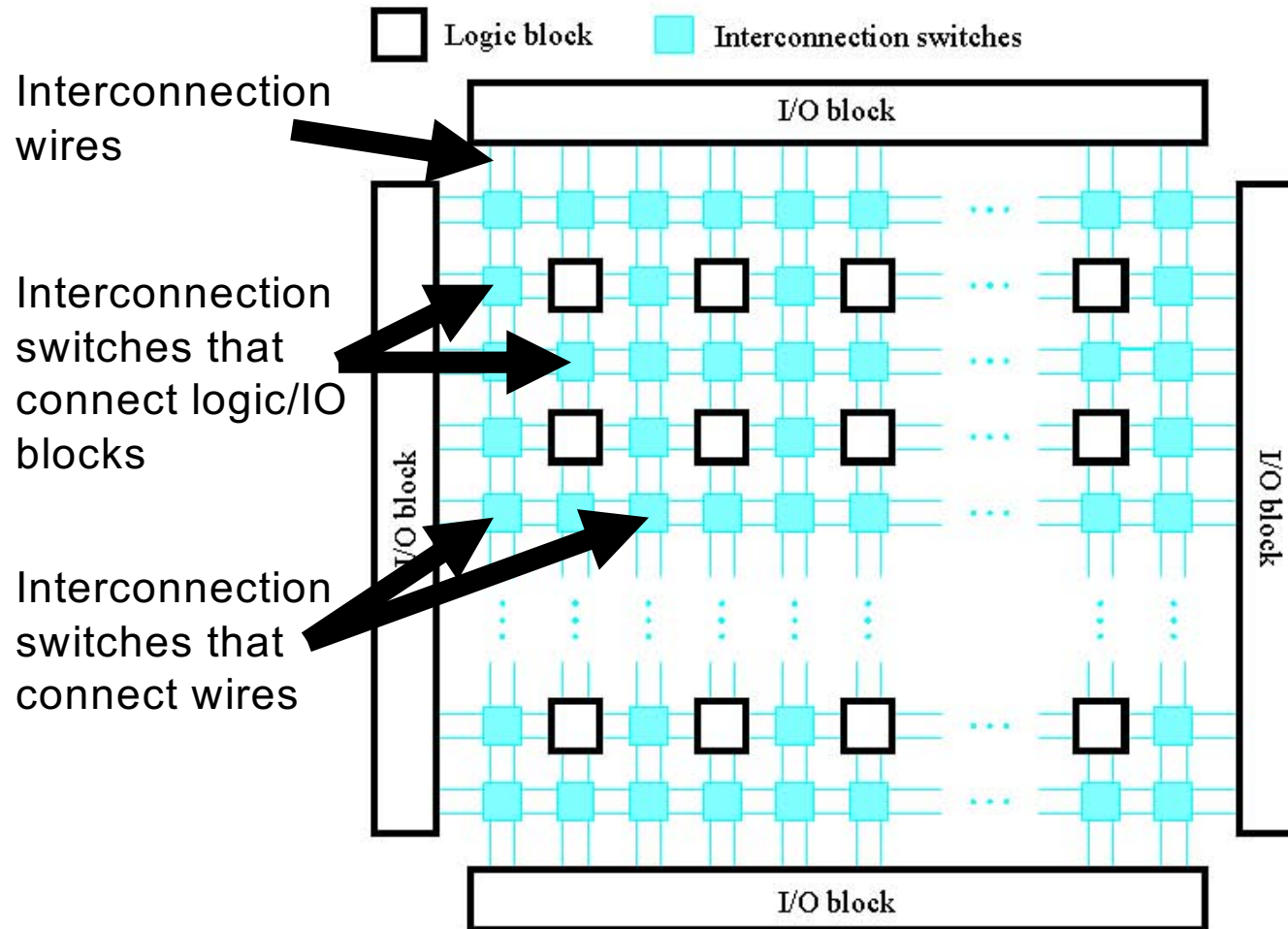


Programmable (Configurable) Logic Block

 - PLB (or CLB), like in SPLD and CPLD, macrocell is added to provide more flexibility




Look Up Table (LUT)

- A typical PLB has a LUT
- Each LUT contains 2^N storage cells, N is the number of inputs to the LUT
 - **SRAM** for storage cell
 - Each storage cell can hold a value, either “1” or “0”
 - The cells are programmed to implement particular logic functions
 - The cells may be reconfigured to implement a different logic function in the same LUT
- N input LUT can implement any N variable logic function

 

LUT Example

 
- Implement the logic function specified by the truth table using a 2-input LUT



Static RAM (SRAM) Cell


- Static Random Access Memory (SRAM) cell

SRAM cell

 


- Dynamic RAM (DRAM) cell

DRAM cell

 


3-input LUT

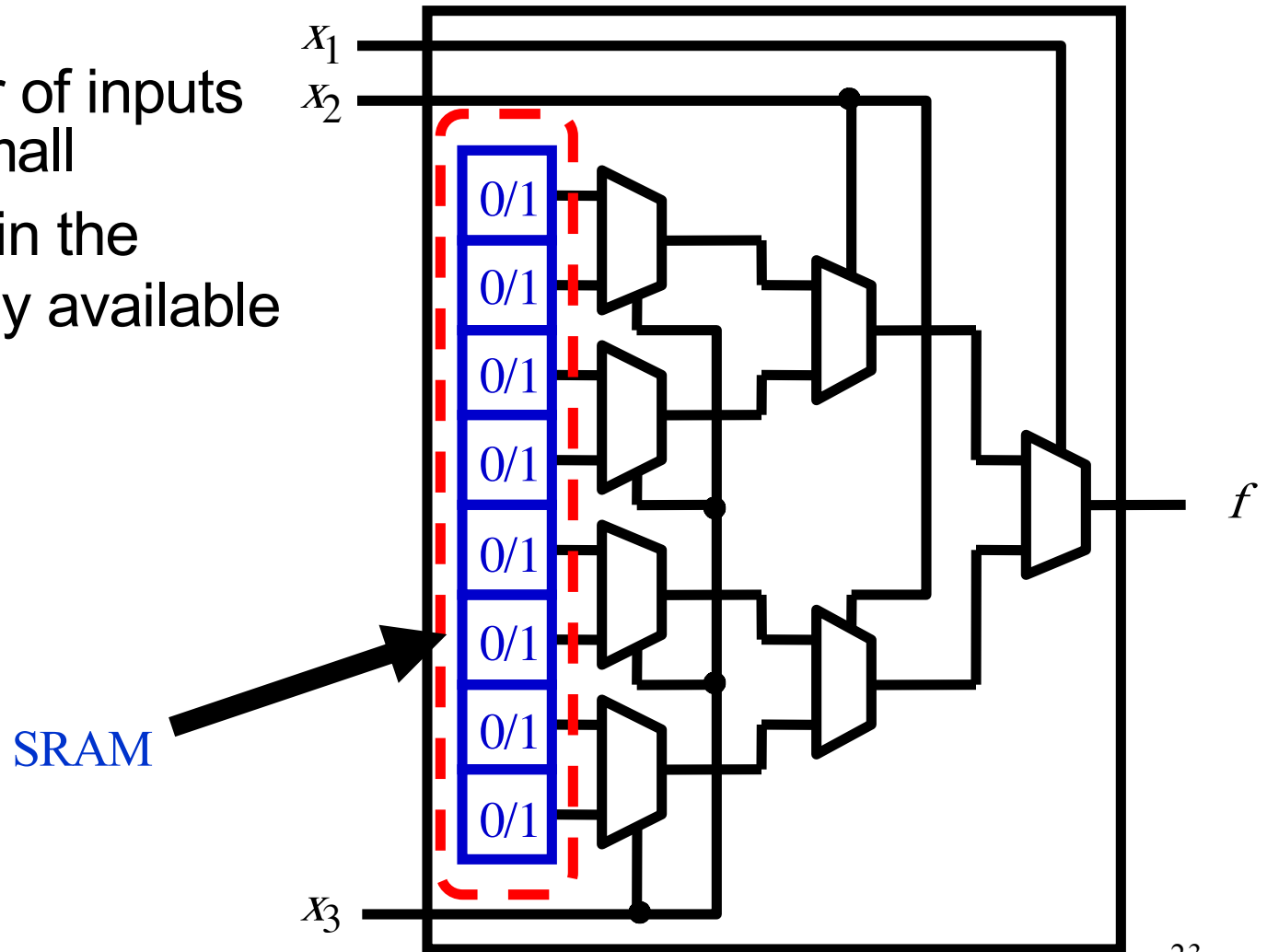- The number of inputs to LUT is small
- 4 - 6 inputs in the commercially available FPGAs




FPGA Internals: Lookup Tables (LUTs)


- Partitioning among smaller LUTs is more size efficient
 - Example: 9-input circuit

 

Original 9-input circuit

 


Partitioned among
3x1 LUTs

 

Requires only 4
3-input LUTs
(8x1 memories) –
much smaller than
a 9-input LUT
(512x1 memory)


Logic Implemented with LUTs

- Circuits with more inputs

 


2-Output LUTs

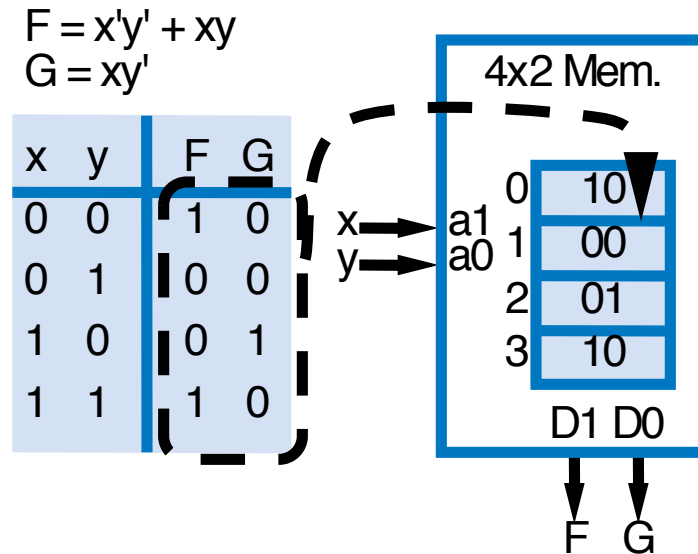- LUT typically has 2 (or more) outputs, not just one




2-Output LUTs

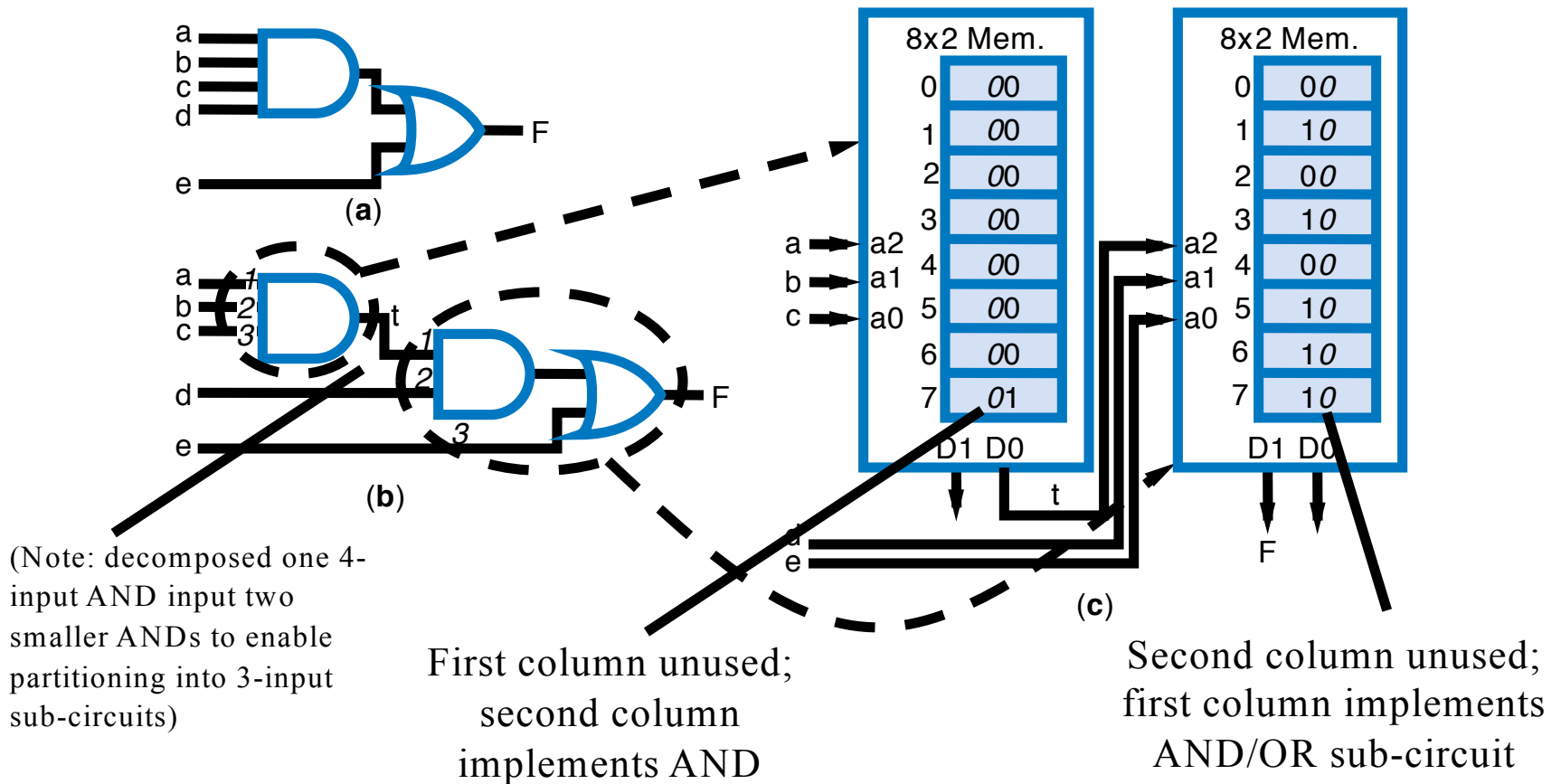- Example: Partitioning a circuit among 3-input 2-output lookup tables




2-Output LUTs

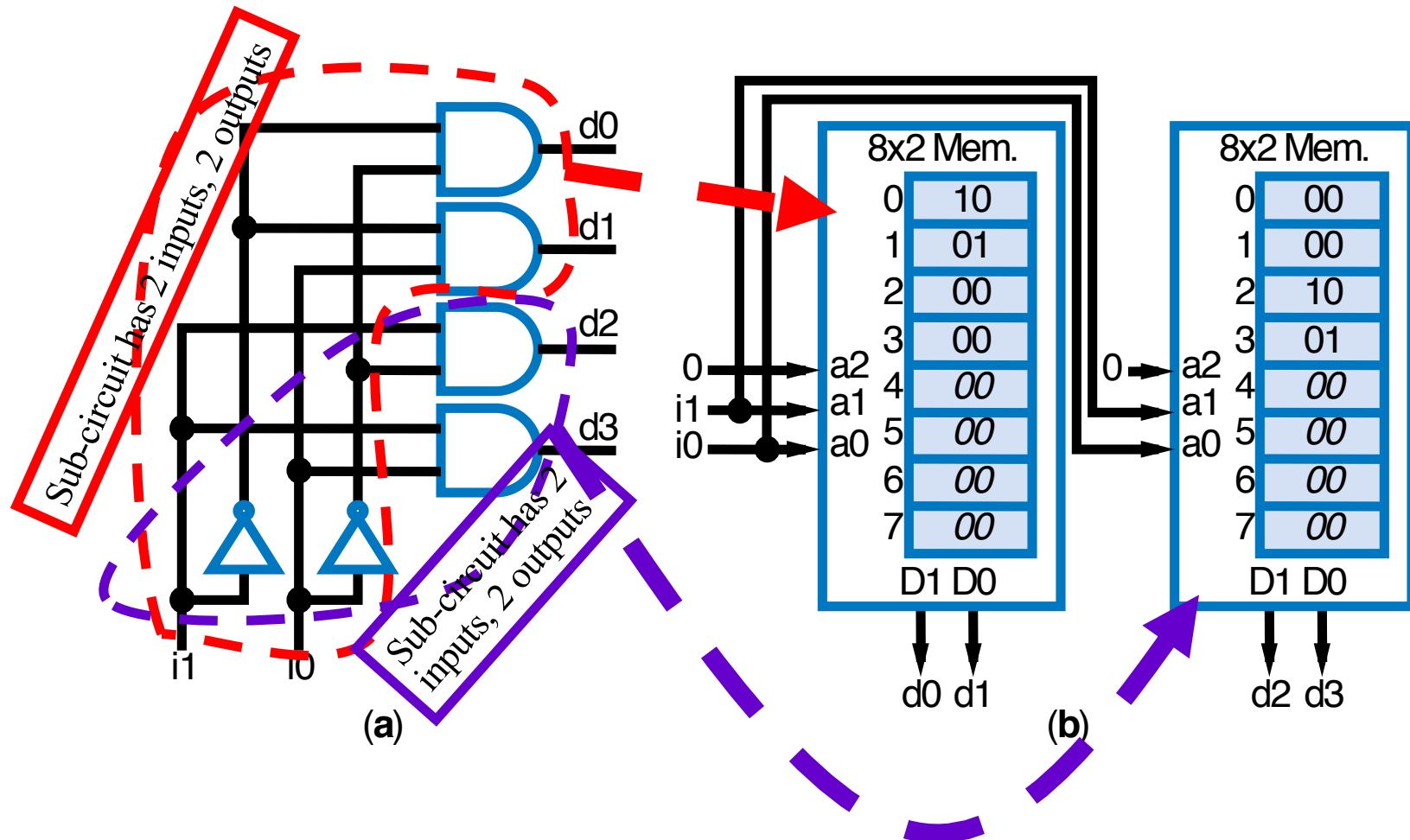- Example: Mapping a 2x4 decoder to 3-input 2-output LUTs




FPGA Configuration Example

 - Blue x indicates a connection
- $f_1 = x_1x_2$
- $f_2 = x_2'x_3$
- $f = f_1 + f_2$




Xilinx Spartan 3 FPGA CLB Structure

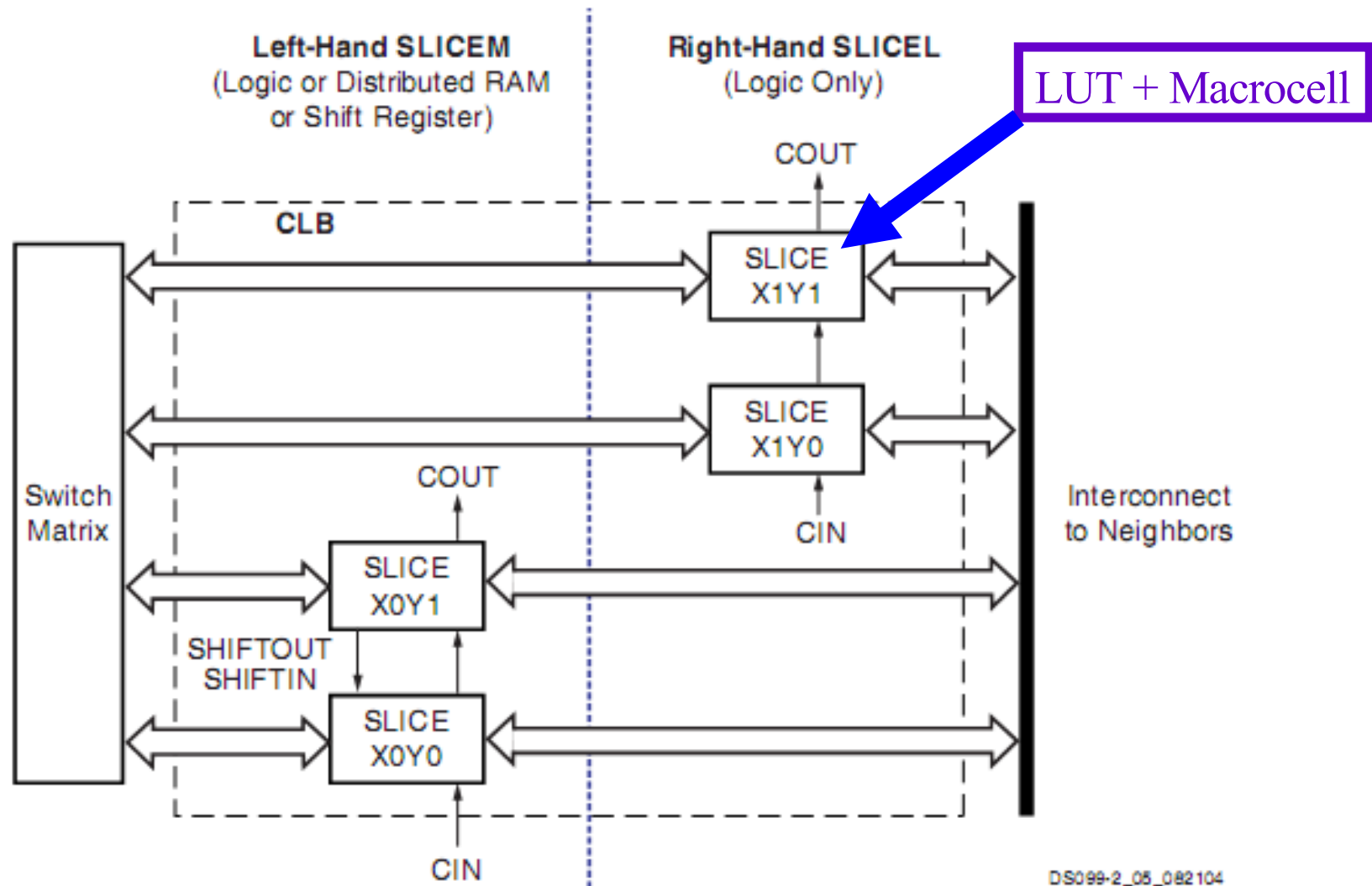


Courtesy of Xilinx Inc.


Xilinx FPGA Switches and Wires

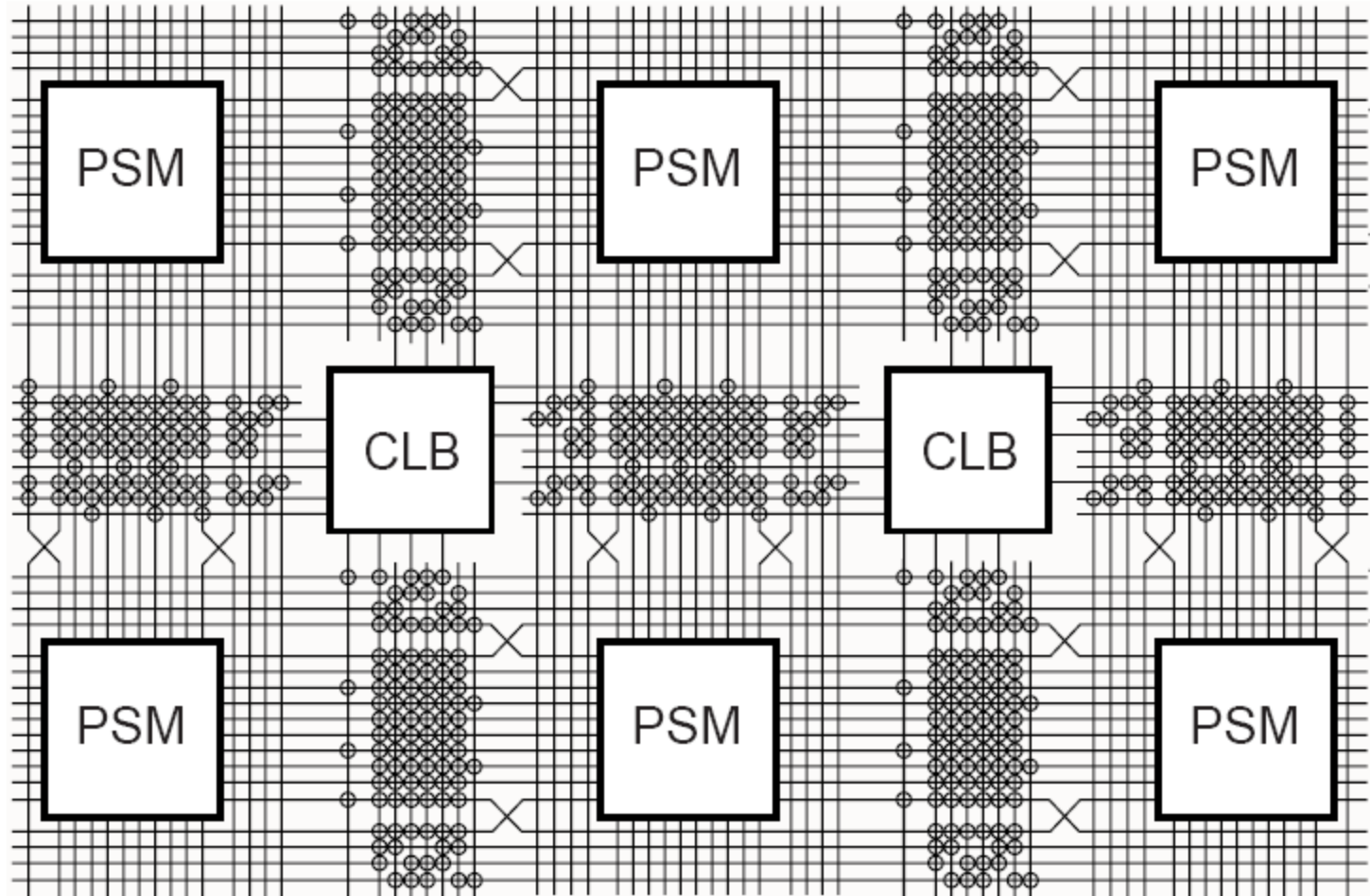

Programmable Switch

 


Xilinx FPGA PSM

 

Programmable Switch Matrix (PSM)


Basic I/O Block Structure

 


Advanced FPGA Features

- Dozens of millions of equivalent logic gates
- Enhanced clock features
- Flexible embedded memory blocks
- Intellectual property (IP) cores
- Embedded processors (hard and soft)
- Digital signal processing (DSP) blocks, tools, design flows (specific FPGA vendors)
- Dedicated hardware multipliers
- high-speed communication capabilities
- Advanced I/O standards and protocol support

FPGA Example – Spartan 3

 

Example of FPGA Implementation

 

Pros and Cons of FPGA

- Pros
 - Fast turnaround.
 - Low NRE (non-recurring engineering) cost.
 - Low risk.
 - Effective design verification.
 - Low testing cost.
- Cons (compare to regular IC chip implementation, and are improving)
 - *Bigger chip size*
 - *Higher cost*
 - *Higher power consumption*
 - *Slower speed*
- Technology is still advancing