

Summer-2019 UM-SJTU JI Ve311 Homework #2

Instructor: Dr. Chang-Ching Tu


Due: 10:00 am, June 13, 2019 (Thursday) in class

Note:

- (1) Please use A4 size papers.
- (2) Please use the SPICE model below for simulation.

```
.model Dbreak D Is=1e-14 Rs=0 N=1 TT=0 Cjo=0pF
```

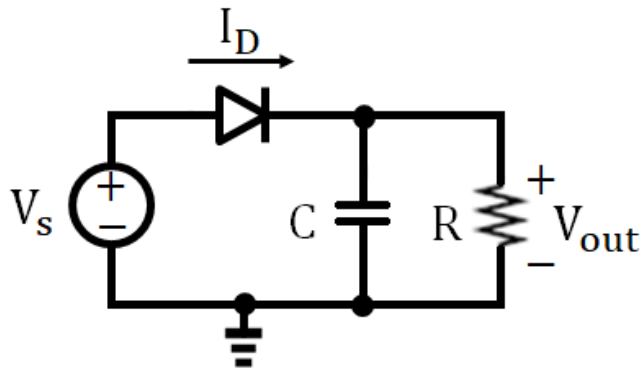1. [Half-Wave Rectifier] Design a half-wave rectifier circuit, such as below, which can convert a sinusoidal voltage input, $V_s = 5\sin(2\pi 60 \cdot \text{time})$, to an almost constant voltage output.
 - (a) [20%] Assuming $V_{on} = 0.7 \text{ V}$ and $R = 5 \text{ k}\Omega$, calculate C which makes the ripple voltage (V_r) is smaller than 0.1 V . Estimate V_{dc} , I_{dc} , θ_c , ΔT , I_{peak} , I_{surge} and PIV of the designed half-wave rectifier.
 - (b) [15%] In Pspice, plot V_s and V_{out} versus time on the sample graph to find out the values of V_{dc} , I_{dc} , V_r and PIV. Comment on the simulation results compared to the hand-calculated ones.
 - (c) [15%] In Pspice, plot I_D versus time to find out the values of I_{peak} and I_{surge} . Comment on the simulation results compared to the hand-calculated ones.



2. [Full-Wave Bridge Rectifier] Design a full-wave bridge rectifier circuit, such as below, which can convert a sinusoidal voltage input, $V_s = 5\sin(2\pi 60 \cdot \text{time})$, to an almost constant voltage output.
- (a) [20%] Assuming $V_{on} = 0.7 \text{ V}$ and $R = 5 \text{ k}\Omega$, calculate C which makes the ripple voltage (V_r) smaller than 0.1 V . Estimate V_{dc} , I_{dc} , θ_c , ΔT , I_{peak} , I_{surge} and PIV of the designed full-wave bridge rectifier.
- (b) [15%] In Pspice, plot V_s (using “voltage differential marker” function) and V_{out} versus time on the sample graph to find out the values of V_{dc} , I_{dc} , V_r and PIV. Comment on the simulation results compared to the hand-calculated ones.
- (c) [15%] In Pspice, plot I_{D2} and I_{D3} versus time on the same graph to find out the values of I_{peak} and I_{surge} . Comment on the simulation results compared to the hand-calculated ones.

