

VE370 HW3

Pan Chongdan 516370910121

1. a. jr instruction should use \$ra instead of \$vo

2. a. int function (int a, int b, int c)

```
int i = a + b;  
if (c != 0) return i;  
i = b - a;
```

3. a. | 0 |

4. a. Executable File Header

	Text size	
	Data size	440 Hex
		90 Hex
Text Segment	Address	instruction
	00400000 Hex	lbu \$a0, 5000(\$gp)
	00400004 Hex	jal 00400000 Hex
	...	
	0040c440 Hex	sw \$a1, 5090(\$gp)
	00400444 Hex	jal 00400440 Hex
Data Segment	Address	Symbol
	10000000 Hex	X
	10000004 Hex	B
	10000010 Hex	Y
	10000094 Hex	A

5. a. Yes, the text size and data size can't exceed 440 Hex and 90 Hex

6. a. Since the text segment has address for each instruction, the address must be within the text size, or branch and jump instruction may jump out of the allocated size and cause problems for assemblers.


Problem 7

Verilog code

```
module HW3_1(clock, A, B, F, sel);
    input [31:0]A;
    input [31:0]B;
    input sel;
    input clock;
    output [31:0]F;
    reg [31:0]F;
    always @(posedge clock)begin
        if(sel==1)begin
            F<=A;
        end
        else begin
            F<=B;
        end
    end
end
endmodule
```

testbench

```
module HW3_1_TEST();
    reg clk, sel;
    reg [31:0]A;
    reg [31:0]B;
    wire [31:0]F;
    HW3_1 UUT(clk, A, B, F, sel);
    initial begin
        #0 clk=0;A=344;B=23;sel=0;;
        #100 A=34;B=283;
        #200 A=0;B=10;
    end
    always #10 clk=~clk;
    always #50 sel=~sel;
endmodule
```

 

Problem8


Verilog Code

```
module HW3_2(clock, a, b, ainvert, binvert, result, carryin, op, set);
input clock;
input a;
input b;
input ainvert;
input binvert;
input carryin;
input [1:0]op;
output result;
output set;
reg result, set, a1, b1;
always @(posedge clock)begin
    if(ainvert==1)a1=~a;
    if(binvert==1)b1=~b;
    set=a1+b1+carryin;
    if(op==0)result=(a&b);
    else if (op==1)result=(a||b);
    else if (op==2)result=set;
    else if(a<b)result=1;
    else result=0;
end
endmodule
```

testbench

```
module HW3_2_TEST();
reg clock;
reg a;
reg b;
reg ainvert;
reg binvert;
reg carryin;
reg [1:0]op;
wire result, set;
HW3_2 UUT(clock, a, b, ainvert, binvert, result, carryin, op, set);
initial begin
    #0 clock=0; ainvert=0; binvert=0; op=0; a=0; b=1; carryin=0;
    #10 ainvert=~ainvert;
    #20 binvert=~binvert;
    #25 ainvert=~ainvert;
    #30 binvert=~binvert; op=1;
    #40 op=2;
    #50 op=3;
    #60 carryin=1;
    #70 op=4;

end
always #2 clock=~clock;
endmodule
```

 

Problem 9

Verilog code

```

3 module HW3_3(RR1, RR2, WR, WD, RD1, RD2, write);
4     input [4:0]RR1;
5     input [4:0]RR2;
6     input [4:0]WR;
7     input [31:0]WD;
8     input write;
9     output [31:0]RD1;
10    output [31:0]RD2;
11    reg [31:0]RD1;
12    reg [31:0]RD2;
13    reg [31:0]REG[31:0];
14    always @(*)begin
15        RD1='b0;
16        RD2='b0;
17        if(write)REG[WR]<=WD;
18        else if(!write)begin
19            RD1<=REG[RR1];
20            RD2<=REG[RR2];
21        end
22    end
23 endmodule
24

```

testbench

```

2
3 module HW3_3_TEST();
4     reg [4:0]RR1;
5     reg [4:0]RR2;
6     reg [4:0]WR;
7     reg [31:0]WD;
8     reg write;
9     wire [31:0]RD1;
10    wire [31:0]RD2;
11    HW3_3 UUT(RR1, RR2, WR, WD, RD1, RD2, write);
12    initial begin
13        #0 write=1;WR=0;WD=0;RR1=0;RR2=0;
14        #5 WR=1;WD=7;
15        #10 WR=3;WD=100;
16        #25 write=0;RR1=1;RR2=3;WR=5;WD=9;
17        #30 RR2=1;RR1=3;
18    end
19 endmodule
20

```

> RR1[4:0]	00	00	01	03
> RR2[4:0]	00	00	03	01
> WR[4:0]	00	00 01 03	05	
> WD[31:0]	00000000	0000 00000064	00000009	
write	1			
> RD1[31:0]	ZZZZZZZZ	ZZZZZZZZ 00000007	00000064	
> RD2[31:0]	ZZZZZZZZ	ZZZZZZZZ 00000064	00000007	