

# Topic 13

## Arithmetic Components

# Components to be discussed

- Arithmetic and logic unit (ALU)
- Carry lookahead adder
- Incrementer
- Magnitude comparator
- Multiplier

# Arithmetic-Logic Unit: ALU

- **ALU**: Component that can perform any of various arithmetic (add, subtract, increment, etc.) and logic (AND, OR, etc.) operations, based on control inputs
- Key component in computer

TABLE 4.2 Desired calculator operations


Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	$S = A + B$	S=00010100
0	0	1	$S = A - B$	S=00001010
0	1	0	$S = A + 1$	S=00010000
0	1	1	$S = A$	S=00001111
1	0	0	$S = A \text{ AND } B$ (bitwise AND)	S=00000101
1	0	1	$S = A \text{ OR } B$ (bitwise OR)	S=00001111
1	1	0	$S = A \text{ XOR } B$ (bitwise XOR)	S=00001010
1	1	1	$S = \text{NOT } A$ (bitwise complement)	S=11110000

# Multifunction Calculator with an ALU

- ALU functions selected by a mux
  - But too many wires
  - Wasted power computing all those operations when at any time you only use one of the results

TABLE 4.2 Desired calculator operations

Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	S = A + B	S=00010100
0	0	1	S = A - B	S=00001010
0	1	0	S = A + 1	S=00010000
0	1	1	S = A	S=00001111
1	0	0	S = A AND B (bitwise AND)	S=00000101
1	0	1	S = A OR B (bitwise OR)	S=00001111
1	1	0	S = A XOR B (bitwise XOR)	S=00001010
1	1	1	S = NOT A (bitwise complement)	S=11110000

 


# Carry-Ripple Adder


- Carry-ripple adder

- 4-bit adder: Adds two 4-bit numbers, generates 5-bit output
  - 5-bit output can be considered 4-bit “sum” plus 1-bit “carry out”
- Can easily build any size adder

carries:	c3	c2	c1	cin	
B:	b3	b2	b1	b0	
A:	+	a3	a2	a1	a0
	<hr/>				
	cout	s3	s2	s1	s0

 


(a)

 


(b)

# Carry-Ripple Adder's Behavior

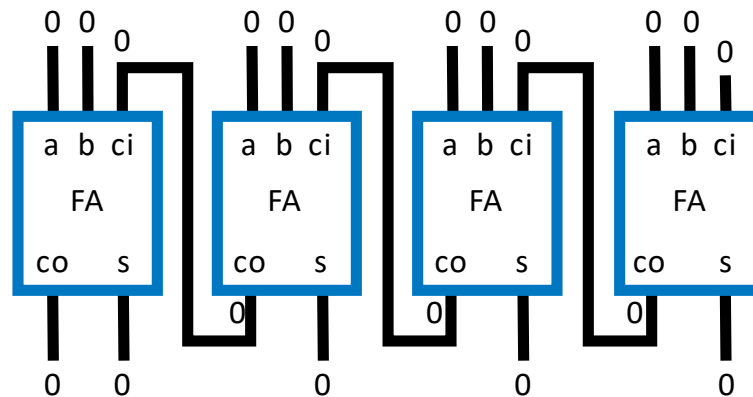

Assume all inputs initially 0

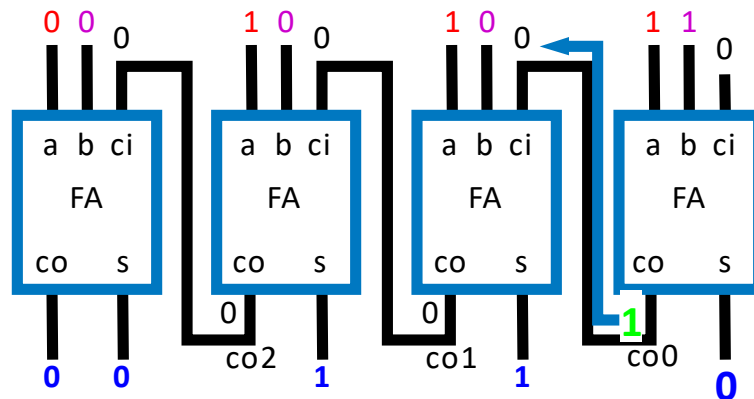


**0111+0001**  
(answer should be 01000)

Output after 2 ns (1 FA delay)


Wrong answer -- something wrong? No -- just need more time for carry to ripple through the chain of full adders.

# Carry-Ripple Adder's Behavior

 


**0111+0001**  
(answer should be 01000)

Outputs after 4ns (2 FA delays)

 

Outputs after 6ns (3 FA delays)


 


Output after 8ns (4 FA delays)

Correct answer appears after 4 FA delays

  
# Faster Adder

- Faster adder – Use two-level combinational logic design process
  - 4-bit two-level adder is big
    - 9 input and 5 output combination circuit
  - Pro: Fast
    - 2 gate-level delays
  - Con: Large
    - Truth table would have  $2^{(4+4+1)} = 512$  rows
    - Plot shows 4-bit adder would use about 500 gates





# Recall Full Adder

 

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}\text{Sum} &= A'B'C + A'BC' + AB'C' + ABC \\ &= \Sigma m(1, 2, 4, 7)\end{aligned}$$

$$\begin{aligned}\text{Carry} &= A'BC + AB'C + ABC' + ABC \\ &= \Sigma m(3, 5, 6, 7)\end{aligned}$$

$$\begin{aligned}\text{Sum} &= A'B'C + A'BC' + AB'C' + ABC \\ &= A'(B'C + BC') + A(B'C' + BC) \\ &= A'(B \oplus C) + A(B \oplus C)'\end{aligned}$$

$$(\text{let } B \oplus C = D)$$

$$= A'D + AD'$$

$$= A \oplus D$$

$$= A \oplus B \oplus C$$

$$\begin{aligned}\text{Carry} &= A'BC + AB'C + ABC' + ABC \\ &= A'BC + AB'C + AB(C' + C) \\ &= A'BC + AB'C + AB\end{aligned}$$

$$= (A'C + A)B + A(B'C + B)$$

$$= (C + A)B + A(C + B)$$

$$= CB + AB + AC + AB$$

$$= AB + AC + BC$$

$$= (A'B + AB')C + AB(C' + C)$$

$$= (A \oplus B)C + AB$$

# Faster Adder – Intuitive Attempt at “Lookahead”

- Produce carries directly

$$c_1 = a_0b_0 + a_0c_0 + b_0c_0$$

$$c_2 = a_1b_1 + a_1c_1 + b_1c_1$$

$$= a_1b_1 + a_1(a_0b_0 + a_0c_0 + b_0c_0) + b_1(a_0b_0 + a_0c_0 + b_0c_0)$$

$$c_3 = a_2b_2 + a_2c_2 + b_2c_2$$

$$= \dots\dots \text{(replace } c_2 \text{)}$$


$$c_4 = a_3b_3 + a_3c_3 + b_3c_3$$

$$= \dots\dots \text{(replace } c_3 \text{)}$$

- Carry outputs of all FAs are represented with  $a_0, a_1, a_2, a_3, b_0, b_1, b_2, b_3$ , and  $c_0$
 
## Faster Adder – Intuitive Attempt at “Lookahead”


- Idea: Modify carry-ripple adder
  - don't wait for carry to ripple, but rather *directly compute* from inputs of earlier stages
  - Called “lookahead” because current stage “looks ahead” at previous stages



Notice – no rippling of carry
 
# Faster Adder – Intuitive Attempt at “Lookahead”

- Carry lookahead logic
  - No waiting for ripple
  - 2-layer SOP logic
- Problem
  - Equations get too big
  - Not efficient
  - Need a better form of lookahead



$$c_1 = b_0c_0 + a_0c_0 + a_0b_0$$

$$c_2 = b_1b_0c_0 + b_1a_0c_0 + b_1a_0b_0 + a_1b_0c_0 + a_1a_0c_0 + a_1a_0b_0 + a_1b_1$$


$$c_3 = b_2b_1b_0c_0 + b_2b_1a_0c_0 + b_2b_1a_0b_0 + b_2a_1b_0c_0 + b_2a_1a_0c_0 + b_2a_1a_0b_0 + b_2a_1b_1 + a_2b_1b_0c_0 + a_2b_1a_0c_0 + a_2b_1a_0b_0 + a_2a_1b_0c_0 + a_2a_1a_0c_0 + a_2a_1a_0b_0 + a_2a_1b_1 + a_2b_2$$

Huge number of gates

# Better Form of Lookahead

- Recall Full Adder, another equation for carry  
Carry =  $ab + (a \oplus b)c$
- Define two terms
  - **Propagate:**  $P = a \oplus b$
  - **Generate:**  $G = ab$
- Compute lookahead carries from  $P$  and  $G$  terms, *not from external inputs*
  - $C_{out} = G + Pc$ 
    - $c_1 = a_0b_0 + (a_0 \oplus b_0)c_0 = G_0 + P_0c_0$
    - $c_2 = a_1b_1 + (a_1 \oplus b_1)c_1 = G_1 + P_1c_1$
    - $c_3 = a_2b_2 + (a_2 \oplus b_2)c_2 = G_2 + P_2c_2$

# Better Form of Lookahead

 

After plugging in:

$$c_1 = G_0 + P_0c_0$$

$$c_2 = G_1 + P_1c_1 = G_1 + P_1(G_0 + P_0c_0)$$

$$c_2 = G_1 + P_1G_0 + P_1P_0c_0$$


$$c_3 = G_2 + P_2c_2 = G_2 + P_2(G_1 + P_1G_0 + P_1P_0c_0)$$

$$c_3 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0c_0$$


$$cout = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$

Much simpler than the intuitive lookahead

# Better Form of Lookahead (cont.)

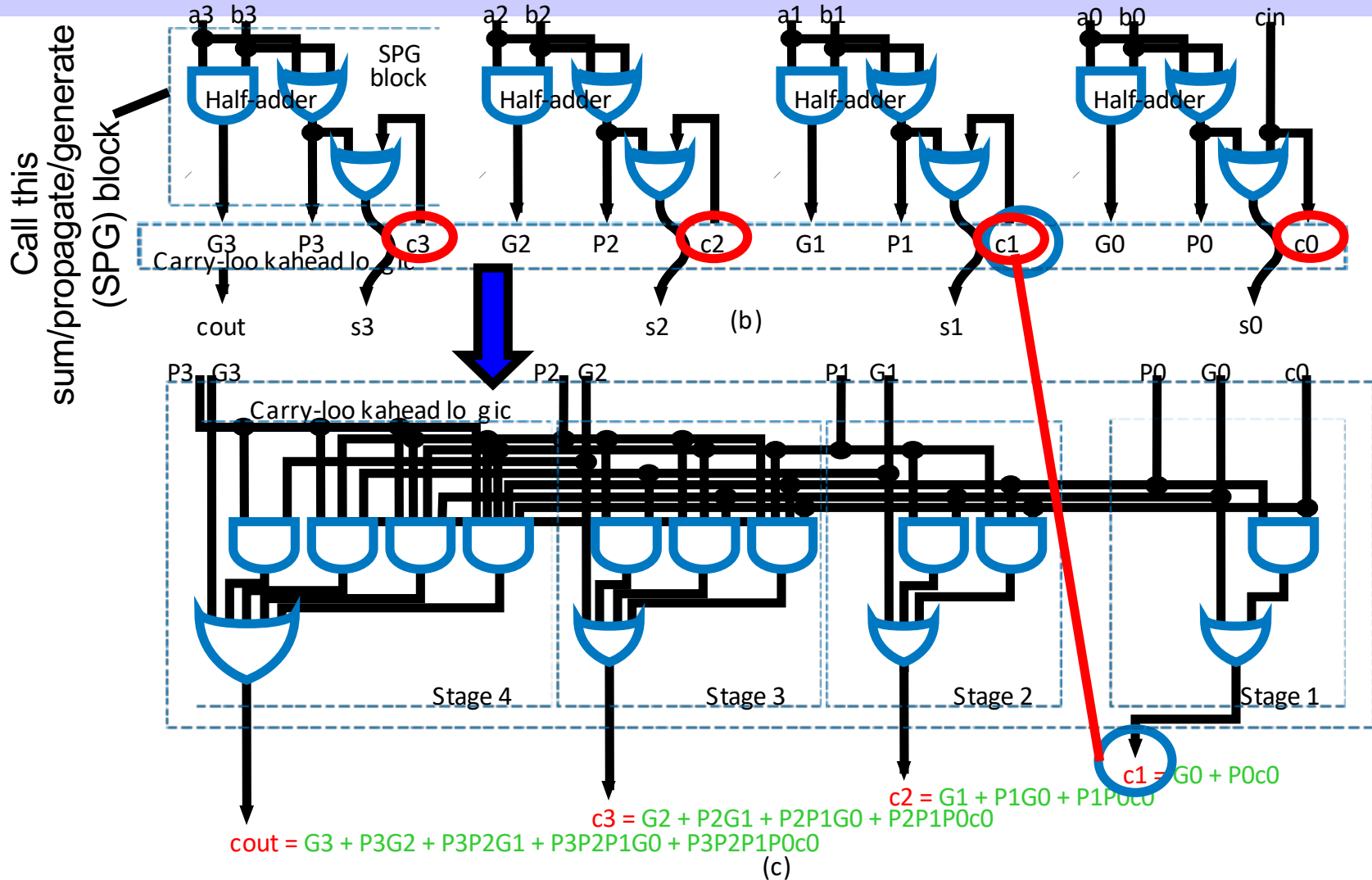


# Better Form of Lookahead (cont.)

 

- With  $P$  &  $G$ , sum outputs are
  - $s_0 = P_0 \oplus c_{in}$
  - $s_1 = P_1 \oplus c_1$
  - $s_2 = P_2 \oplus c_2$
  - $s_3 = P_3 \oplus c_3$



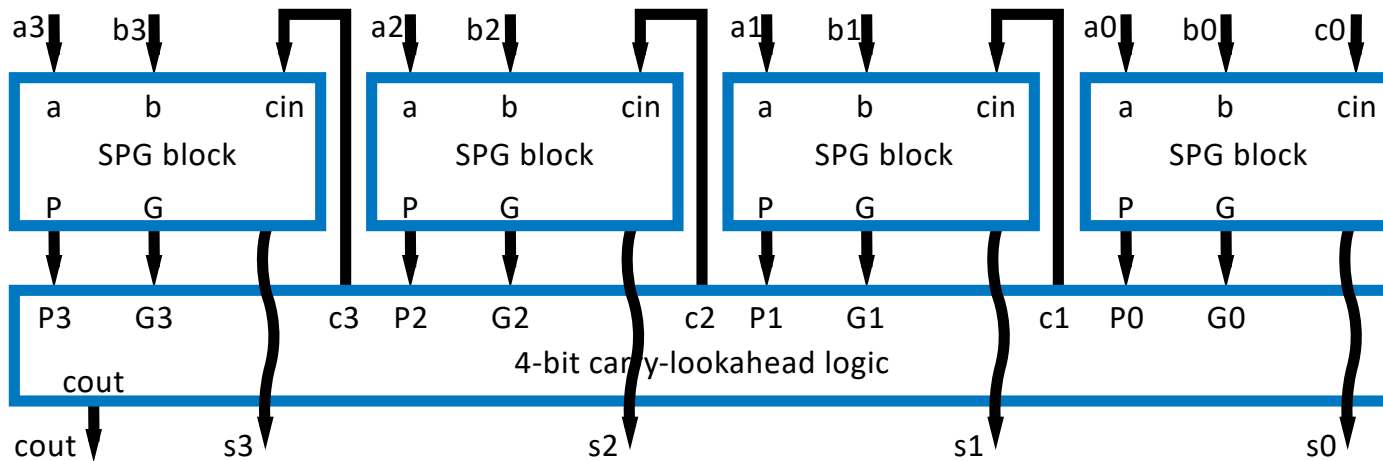
# Carry-Lookahead Adder -- High-Level View



- Fast -- only **4 gate level delays**
  - Each stage has SPG block with 2 gate levels
  - Carry-lookahead logic quickly computes the carry from the propagate and generate bits using 2 gate levels inside
- Reasonable number of gates
- Nice balance between intuitive lookahead and pure combinational logic


# Cascading Adders

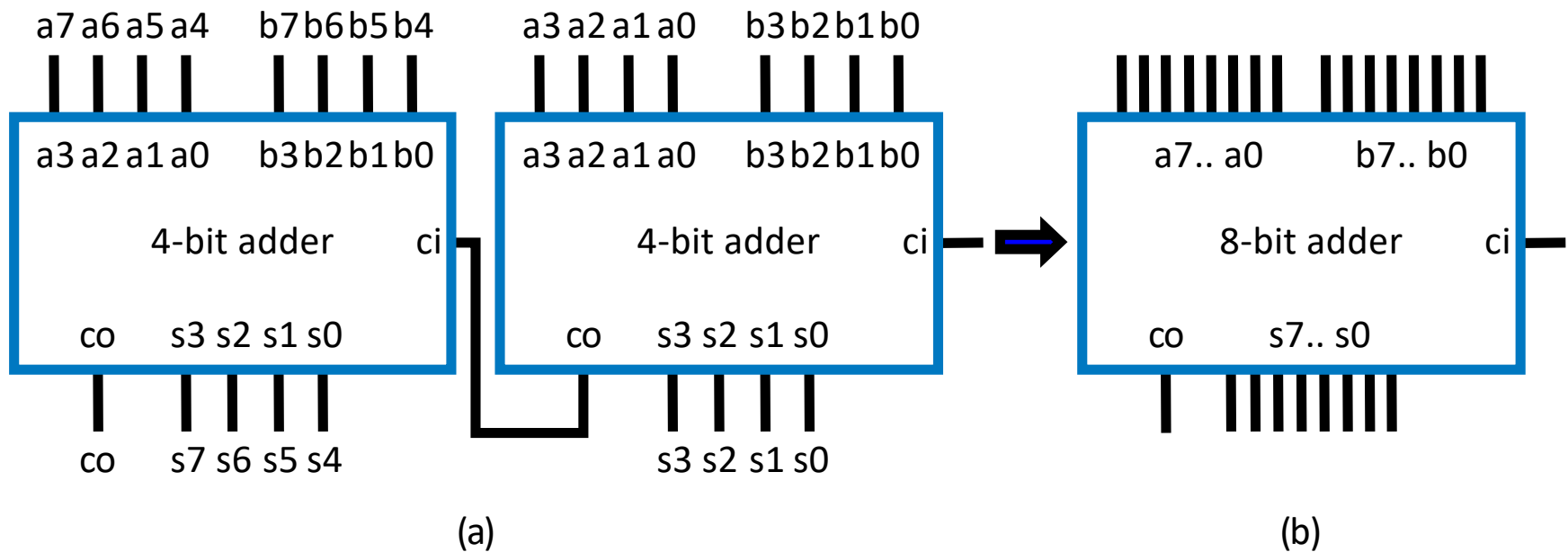- Example: construct an 8-bit adder with two 4-bit adders




# Cascading Adders to CLA Addres

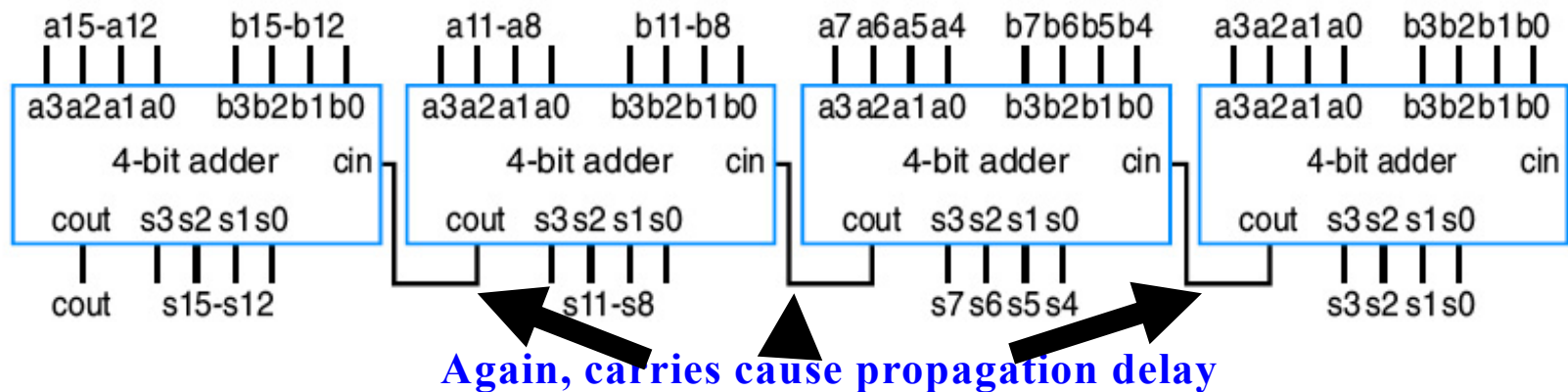- Example: construct an 16-bit adder with four 4-bit adders



# Carry-Lookahead Adder -- High-Level View

- Adding two more outputs: P, G

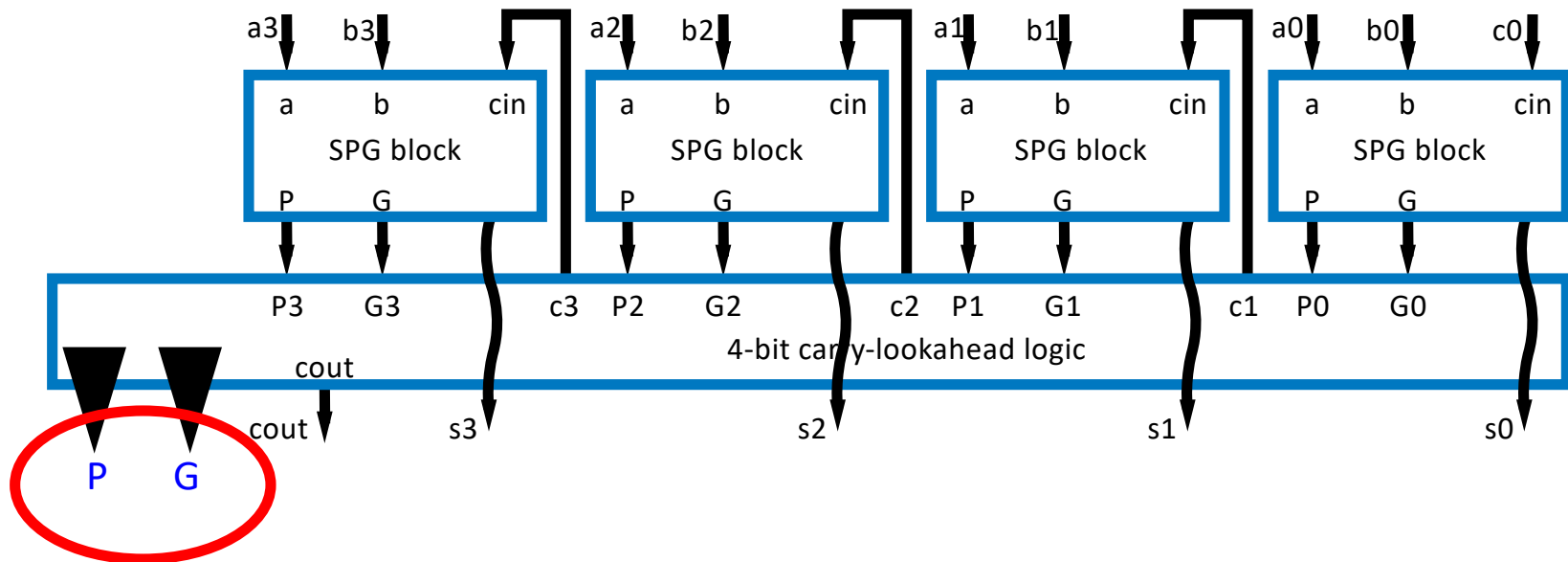


$$P = P_3P_2P_1P_0$$


$$G = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$$

# Cascading Adders to CLA Addres

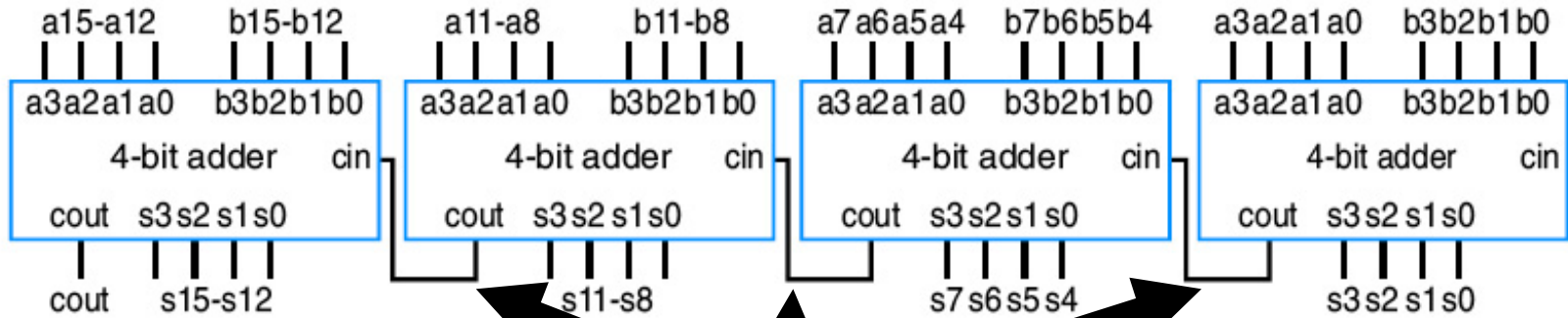- Example: construct an 16-bit adder with four 4-bit adders



Again, carries cause propagation delay

 

$$P = P_3 P_2 P_1 P_0$$

$$G = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$


$$\dots$$

# CLA Adders

- Multi-level CLA structure

 


# CLA Adders

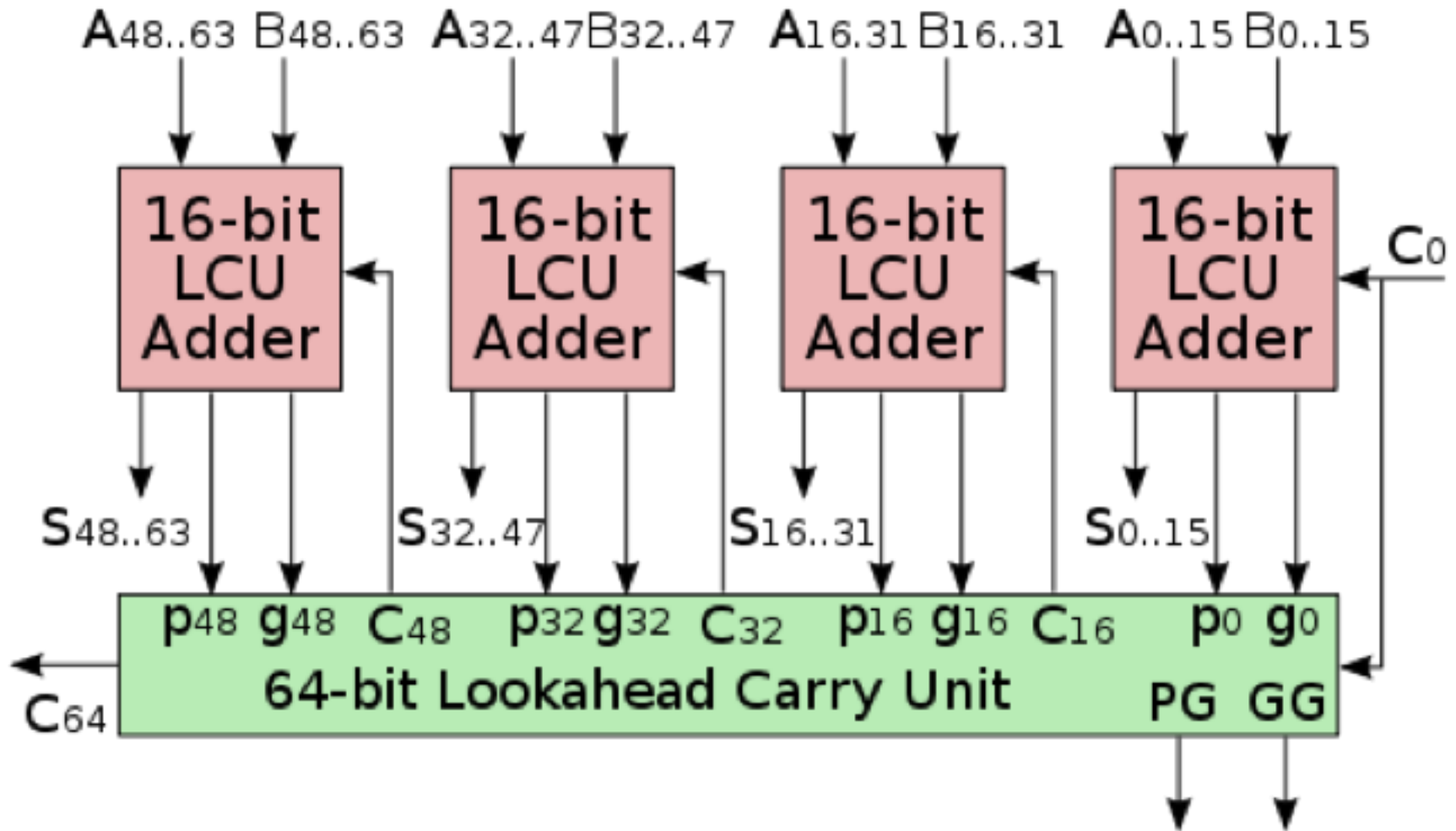
 
# Adder Example: DIP-Switch-Based Adding Calculator

- To prevent spurious values from appearing at output, can place register at output







# Incrementer

- Traditional design procedure
  - Capture truth table
  - Derive equation for each output
    - $c0 = a3a2a1a0$
    - ...
    - $s0 = a0'$
  - Results in small and fast circuit
  - Works for small operand
    - larger operand leads to exponential growth, like for N-bit adder

Inputs				Outputs				
a3	a2	a1	a0	c0	s3	s2	s1	s0
0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	1	0
0	0	1	0	0	0	0	1	1
0	0	1	1	0	0	1	0	0
0	1	0	0	0	0	1	0	1
0	1	0	1	0	0	1	1	0
0	1	1	0	0	0	1	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	1	0
1	0	1	0	0	1	0	1	1
1	0	1	1	0	1	1	0	0
1	1	0	0	0	1	1	0	1
1	1	0	1	0	1	1	1	0
1	1	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	0
 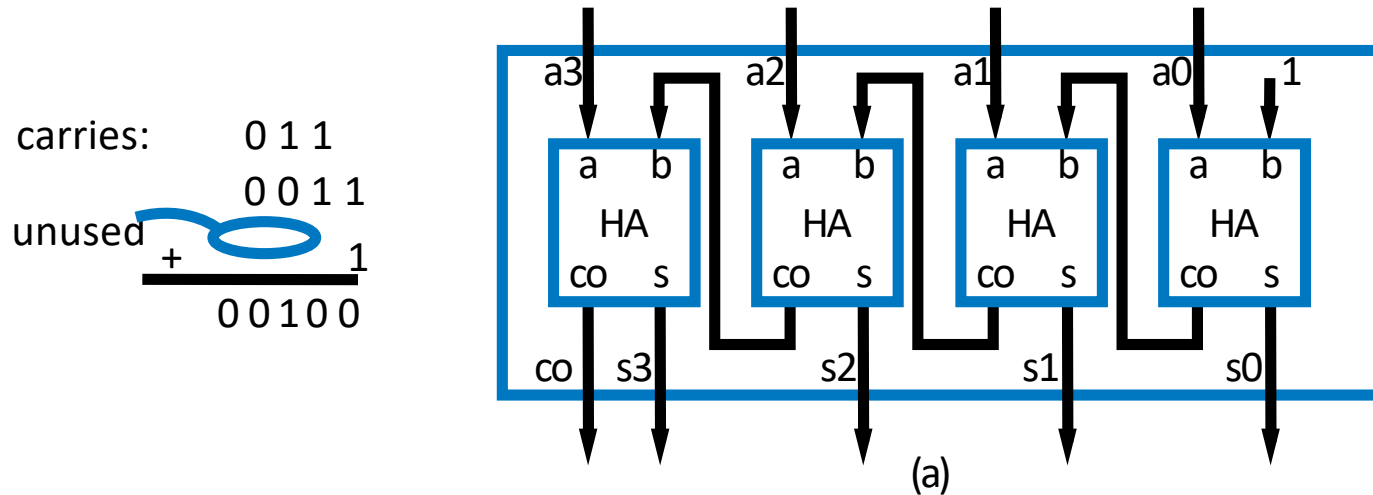
# Incrementer



- Alternative incrementer design
  - Could use N-bit adder with one of the inputs set to 1
  - Use half-adders (adds two bits) rather than full-adders (adds three bits)
  - Slower but simpler



# Comparators

- ***N-bit equality comparator***: Outputs 1 if two N-bit numbers are equal
- Example: 4-bit equality comparator with inputs A and B
  - Approach 1: combinational design procedure
  - Approach 2: recall functionality of XOR and XNOR

0110 = 0111 ?

  

# Magnitude Comparator

- ***N-bit magnitude comparator:***
  - Indicates whether  $A > B$ ,  $A = B$ , or  $A < B$ , for its two N-bit inputs A and B
  - Design approach 1: combinational design procedure
  - Design approach 2: Consider how compare by hand.

A=1011 B=1001

1011    1001 Equal



1011    1001 Equal

1011    1001 Unequal


**So  $A > B$**
 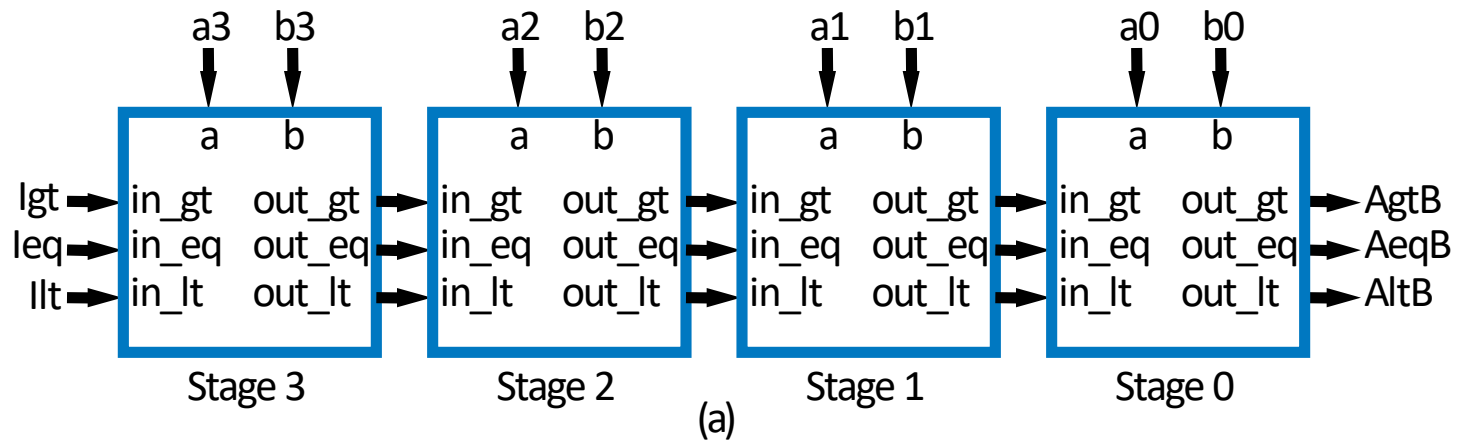
# Magnitude Comparator

- By-hand example leads to idea for design
  - Start at left, compare each bit pair, pass results to the right
  - Each stage has 3 inputs indicating results of higher stage, passes results to lower stage




# Magnitude Comparator

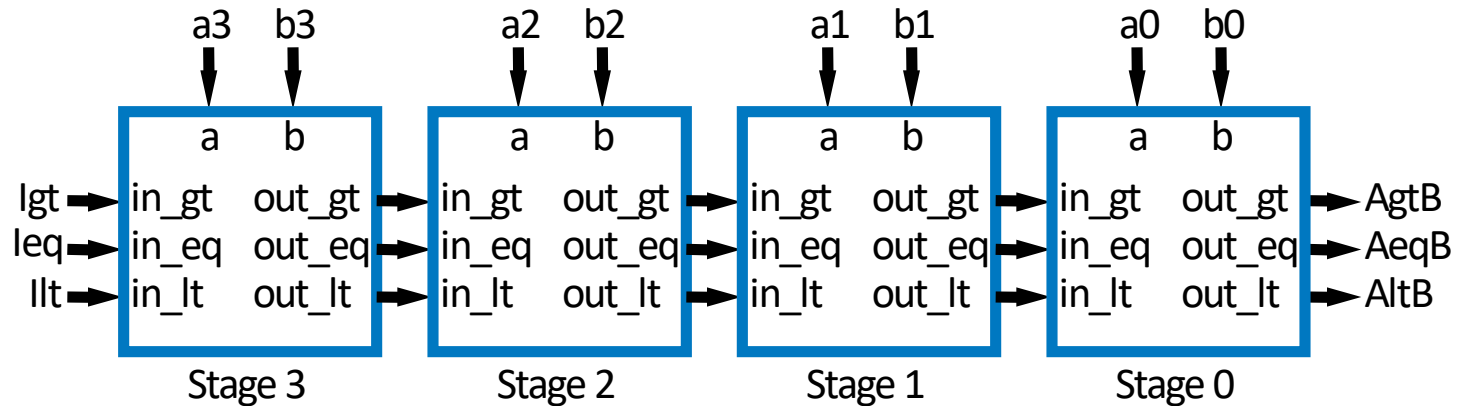

- Each stage:
  - $out\_gt = in\_gt + (in\_eq * a * b')$ 
    - $A > B$  (so far) if already determined in higher stage, or if higher stages equal but in this stage  $a=1$  and  $b=0$
  - $out\_lt = in\_lt + (in\_eq * a' * b)$ 
    - $A < B$  (so far) if already determined in higher stage, or if higher stages equal but in this stage  $a=0$  and  $b=1$
  - $out\_eq = in\_eq * (a \text{ XNOR } b)$ 
    - $A = B$  (so far) if already determined in higher stage and in this stage  $a=b$  too
  - Simple circuit inside each stage, just a few gates (not shown)


# Magnitude Comparator

- How does it work?

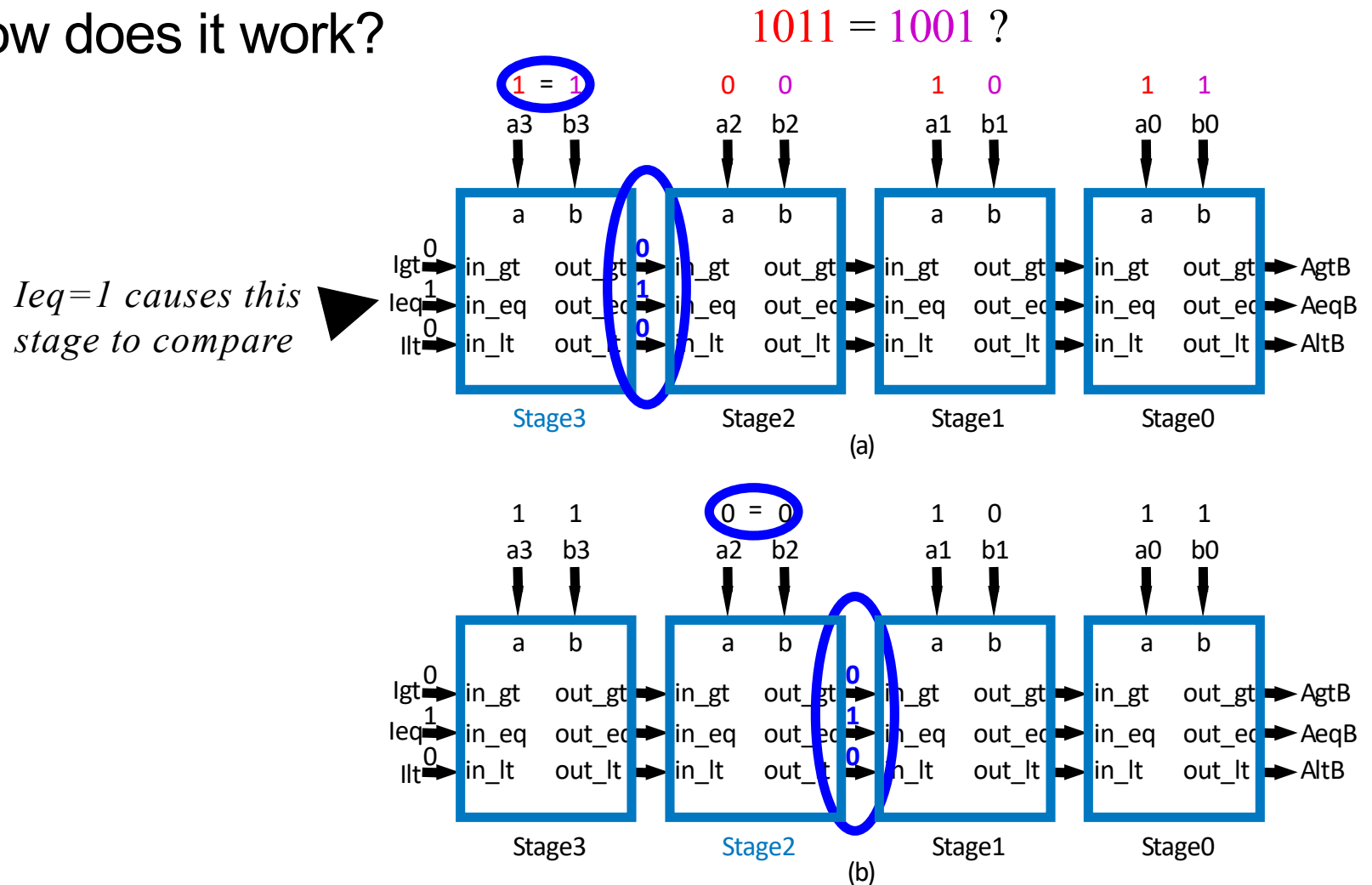


# Magnitude Comparator

1011 = 1001 ?

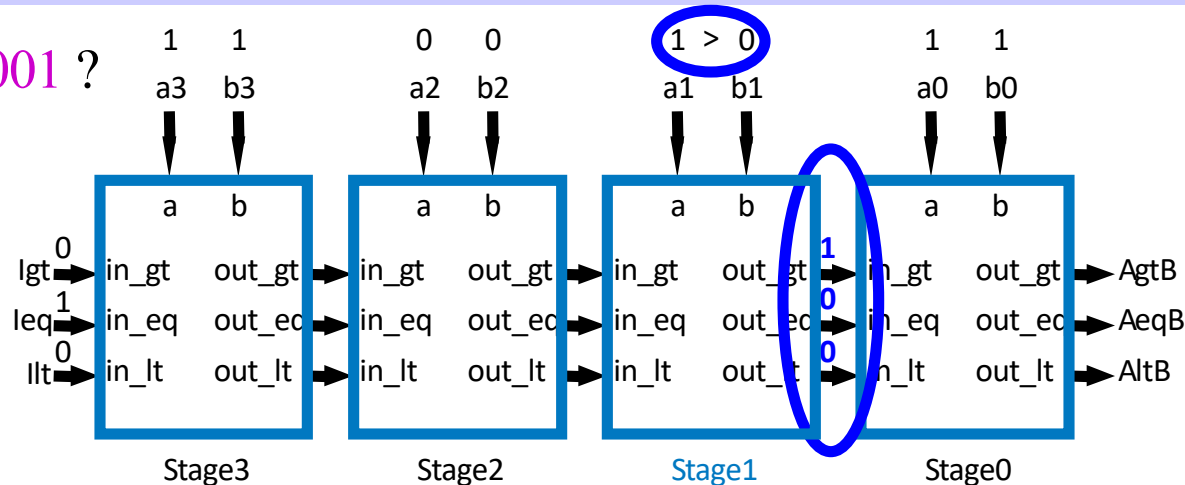

(c)

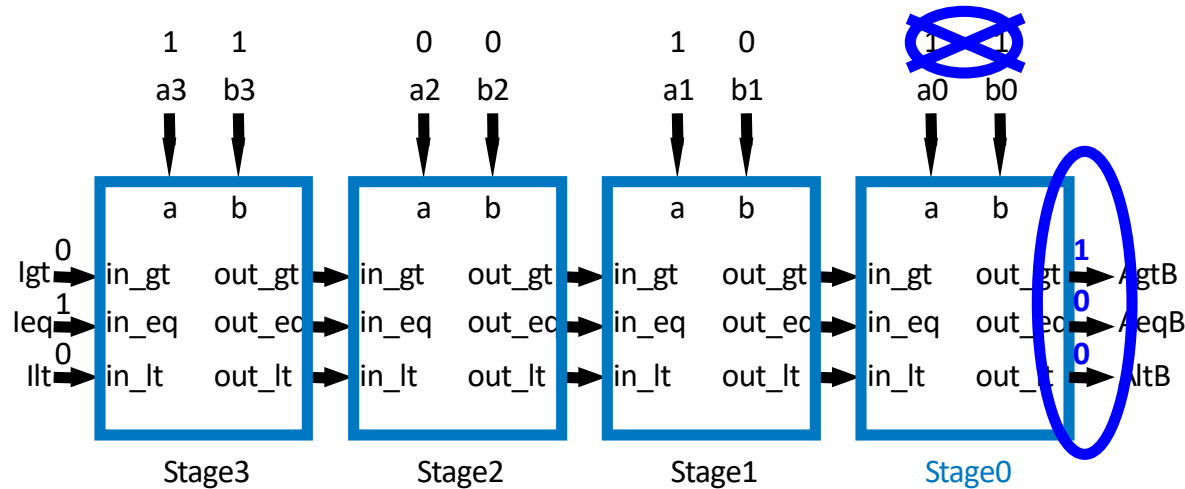



(d)

- Final answer appears on the right
- Takes time for answer to “ripple” from left to right
- Thus called “carry-ripple style” even though there’s no “carry” involved


 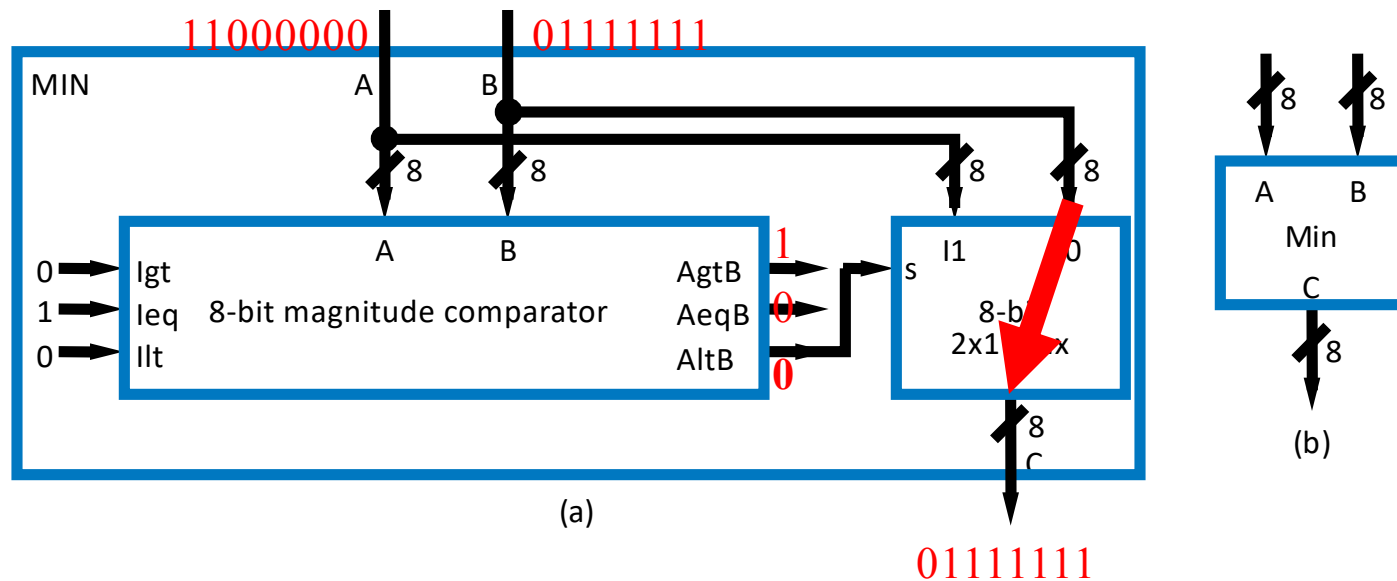
# Magnitude Comparator Example: Minimum of Two Numbers

- Design a combinational component that finds the minimum of two 8-bit numbers
  - Solution: Use 8-bit magnitude comparator and 8-bit 2x1 mux
    - If  $A < B$ , pass A through mux. Else, pass B.



What if inputs are 2's complement???