

VE215 FA2017 Assignment 1

1.6 The charge entering a certain element is shown in Fig. 1.23. Find the current at:

- (a) $t = 1$ ms (b) $t = 6$ ms (c) $t = 10$ ms

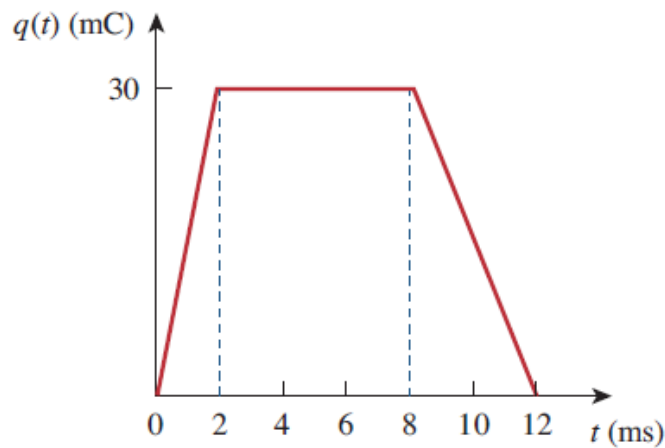


Figure 1.23

For Prob. 1.6.

1.8 The current flowing past a point in a device is shown in Fig. 1.25. Calculate the total charge through the point.

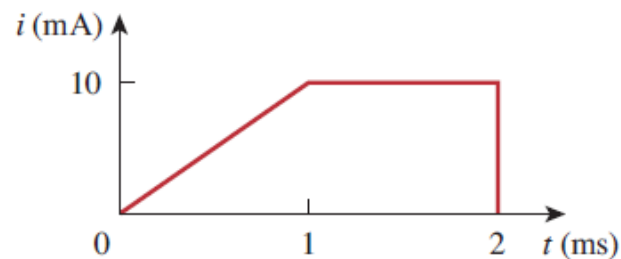


Figure 1.25

For Prob. 1.8.

1.10 A lightning bolt with 10 kA strikes an object for $15 \mu\text{s}$. How much charge is deposited on the object?

- 1.17 Figure 1.28 shows a circuit with five elements. If $p_1 = -205 \text{ W}$, $p_2 = 60 \text{ W}$, $p_4 = 45 \text{ W}$, $p_5 = 30 \text{ W}$, calculate the power p_3 received or delivered by element 3.

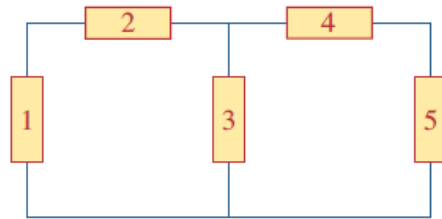


Figure 1.28

For Prob. 1.17.

- 2.14 Given the circuit in Fig. 2.78, use KVL to find the branch voltages V_1 to V_4 .

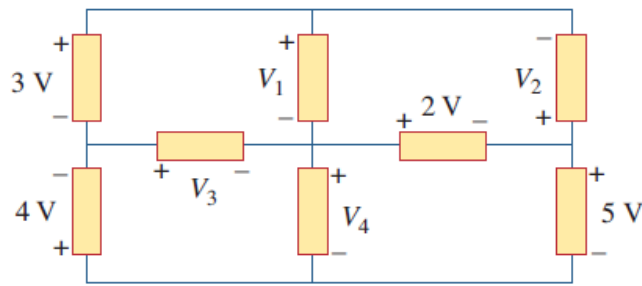


Figure 2.78

For Prob. 2.14.

- 2.21 Find V_x in the circuit of Fig. 2.85.

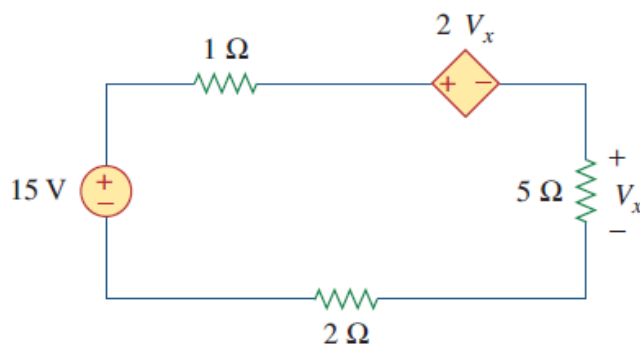


Figure 2.85

For Prob. 2.21.

2.37 Find R for the circuit in Fig. 2.101.

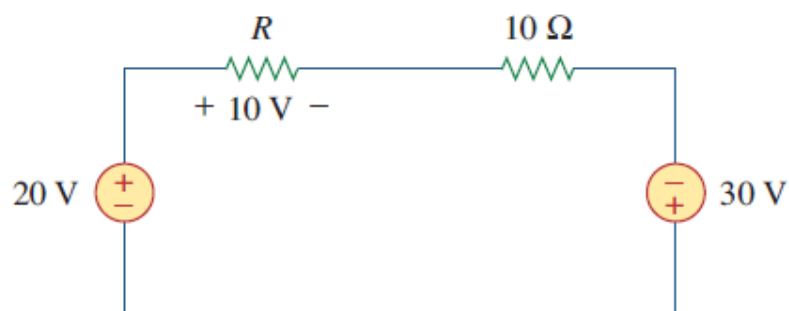


Figure 2.101

For Prob. 2.37.

2.46 Find I in the circuit of Fig. 2.110.


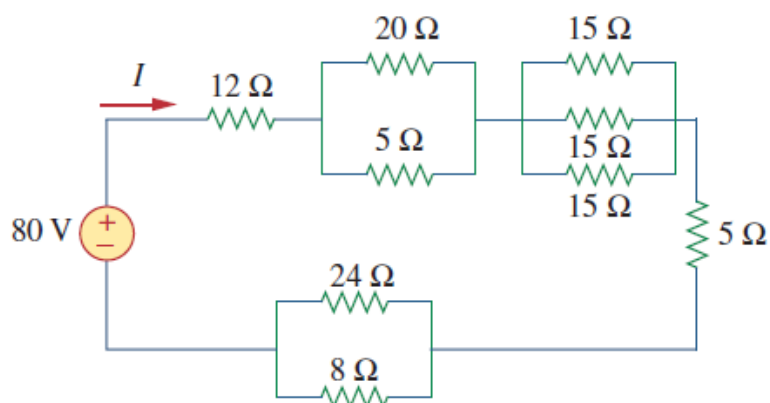



Figure 2.110

For Prob. 2.46.

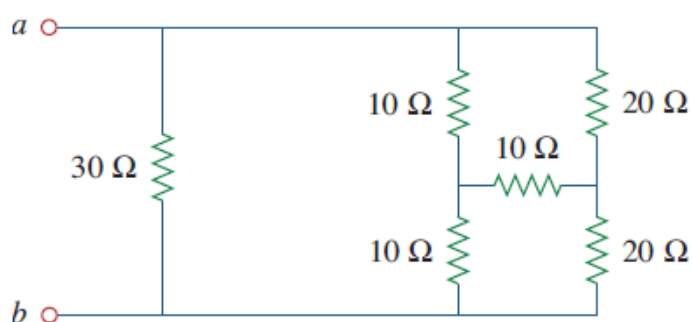2.51 Obtain the equivalent resistance at the terminals a - b for each of the circuits in Fig. 2.115.



(a)

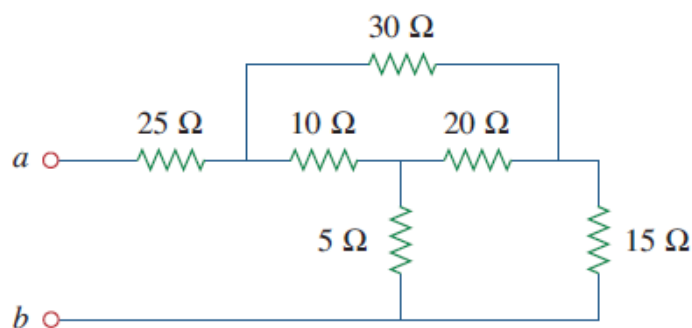

(b)

Figure 2.115

For Prob. 2.51.