

- 12.3 Determine the phase sequence of a balanced three-phase circuit in which $V_{bn} = 440\angle 130^\circ \text{ V}$ and $V_{cn} = 440\angle 10^\circ \text{ V}$. Obtain V_{an} .
- 12.7 Obtain the line currents in the three-phase circuit of Fig. 12.42 on the next page.

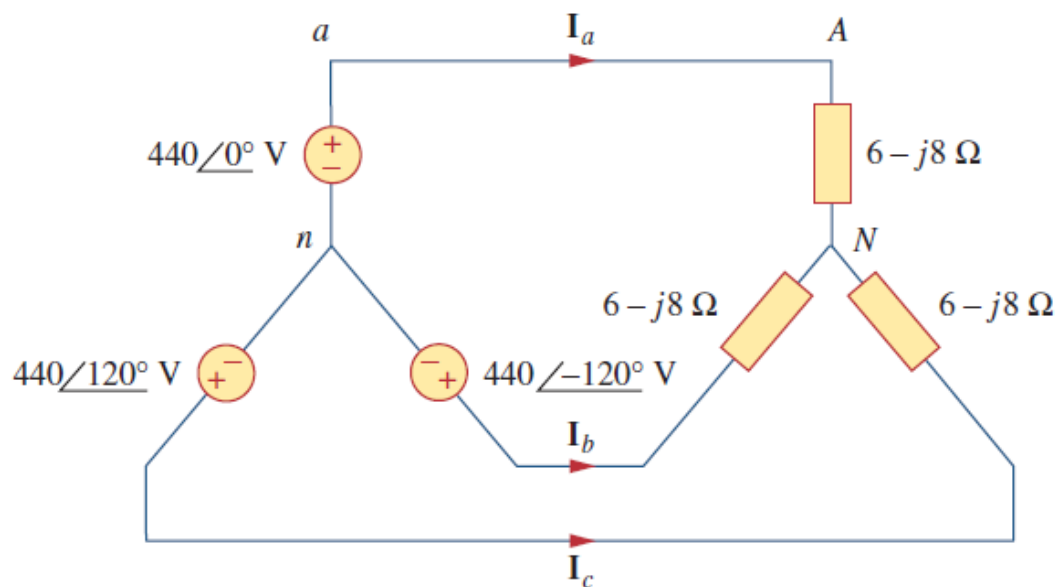


Figure 12.42
For Prob. 12.7.

- 12.11** In the Y- Δ system shown in Fig. 12.44, the source is a positive sequence with $V_{an} = 240\angle 0^\circ$ V and phase impedance $Z_p = 2 - j3\ \Omega$. Calculate the line voltage V_L and the line current I_L .

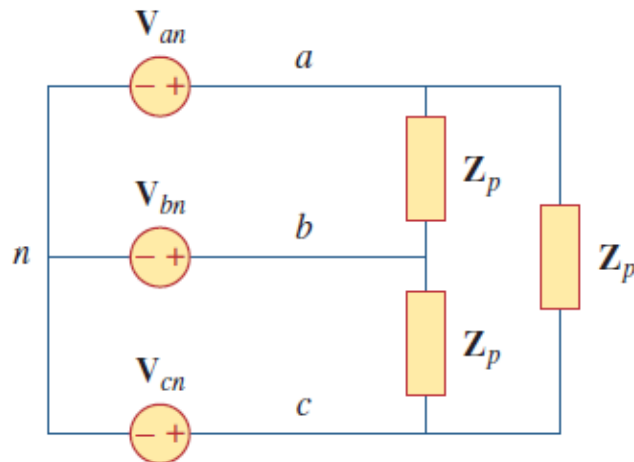



Figure 12.44

For Prob. 12.11.

-  **12.22** Find the line currents I_a , I_b , and I_c in the three-phase network of Fig. 12.53 below. Take $Z_\Delta = 12 - j15\ \Omega$, $Z_Y = 4 + j6\ \Omega$, and $Z_l = 2\ \Omega$.

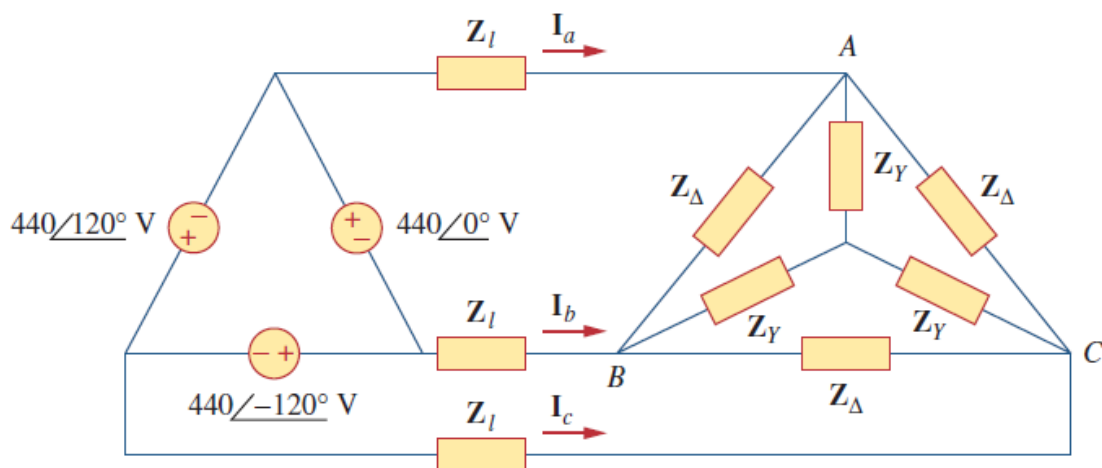


Figure 12.53

For Prob. 12.22.

- 12.31** A balanced delta-connected load is supplied by a 60-Hz three-phase source with a line voltage of 240 V. Each load phase draws 6 kW at a lagging power factor of 0.8. Find:
- (a) the load impedance per phase
 - (b) the line current
 - (c) the value of capacitance needed to be connected in parallel with each load phase to minimize the current from the source
- 12.33** A three-phase source delivers 4.8 kVA to a wye-connected load with a phase voltage of 208 V and a power factor of 0.9 lagging. Calculate the source line current and the source line voltage.
- 12.55** A three-phase supply, with the line voltage 240 V rms positively phased, has an unbalanced delta-connected load as shown in Fig. 12.62. Find the phase currents and the total complex power.

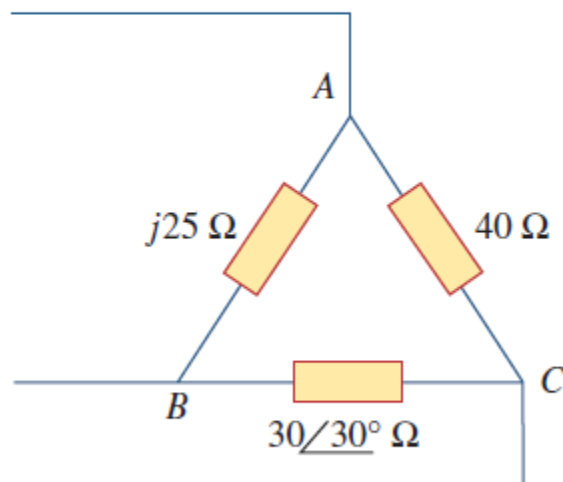


Figure 12.62
For Prob. 12.55.

12.66 A three-phase, four-wire system operating with a 208-V line voltage is shown in Fig. 12.71. The source voltages are balanced. The power absorbed by the resistive wye-connected load is measured by the three-wattmeter method. Calculate:

- (a) the voltage to neutral
- (b) the currents I_1 , I_2 , I_3 , and I_n
- (c) the readings of the wattmeters
- (d) the total power absorbed by the load

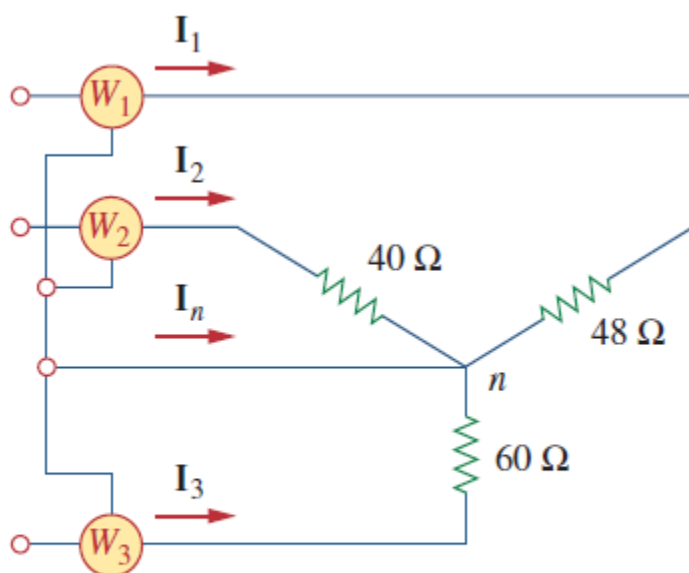


Figure 12.71

For Prob. 12.66.