

Topic 9




Register & Shifter

Introduction

- Two major subsystems in typical digital system
 - Controller
 - Controller generates signals to control datapath based on environment event or state
 - Datapath
 - Datapath routes data to particular destination device according to control signals generated by controller
- This chapter introduces numerous datapath components, and simple datapaths


Registers

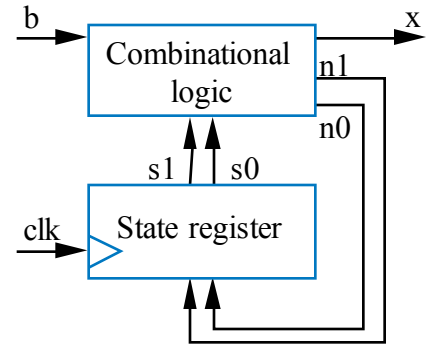  - Can store data, very common in datapaths
- Basic register: Loaded every cycle
 - Useful for implementing FSM -- stores encoded state
 - For other uses, may want to load only on certain cycles





Verilog Modeling of Registers
 
```
module Reg_N_bits (Q, Din, clock);  
  parameter size = 4;  
  input clock;  
  input [size-1:0] Din;  
  output [size-1:0] Q;  
  
  reg Q;  
  
  always @ (posedge clock)  
  begin  
    Q <= Din;  
  end  
endmodule
```



Register with Parallel Load

 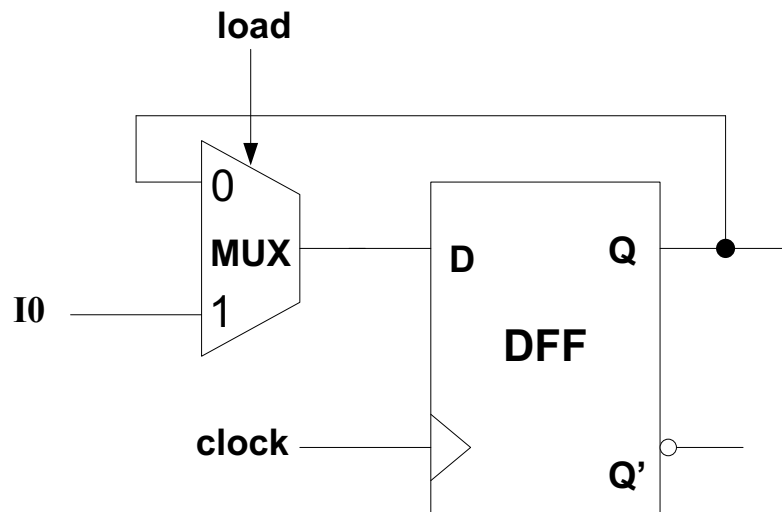
- Add 2x1 mux to each flip-flop
- Register's load input selects mux input to pass
 - Either existing flip-flop value, or new value to load



Synchronous active high Load

Verilog Modeling of Registers
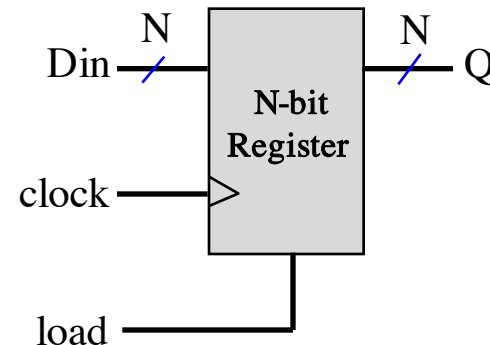
```
module Reg_N_bits (Q, Din, clock, load);  
  parameter size = 4;  
  input clock, load;  
  input [size-1:0] Din;  
  output [size-1:0] Q;  
  
  reg Q;  
  
  always @ (posedge clock)  
  begin  
    if (load) Q <= Din;  
  end  
endmodule
```



Verilog Testbench for Register

```
module Test_Banch;
    parameter half_period = 50;
    parameter reg_size = 3;

    wire [reg_size-1:0] Q;
    reg  [reg_size-1:0] Din;
    reg                                clock, load;


    Reg_N_bits #(reg_size) UUT (Q, Din, clock, load);

    initial begin
        #0    clock = 0; Din = 0;
        #200 Din = 5; load = 1;
        #100 load = 0;
        #200 Din = 3;
        #200 load = 1;
    end

    always #half_period clock = ~clock;


    initial #1000 $stop;
endmodule
```

Timing Diagram from Simulation

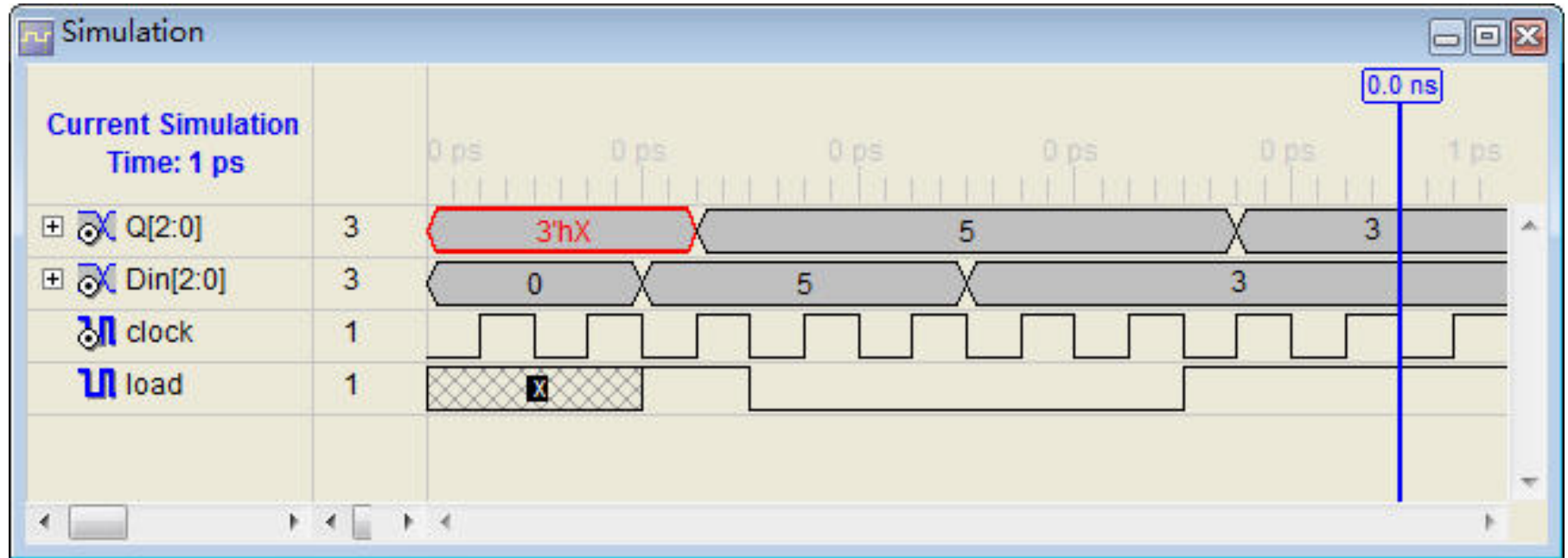


Register Example using the Load Input: Weight Sampler

 
- Scale has two displays
 - Present weight
 - Saved weight
 - Useful to compare present item with previous item
- Use register to store weight
 - Pressing button causes present weight to be stored in register
 - Register contents always displayed as “Saved weight,” even when new present weight appears



Register Example: Above-Mirror Display

 


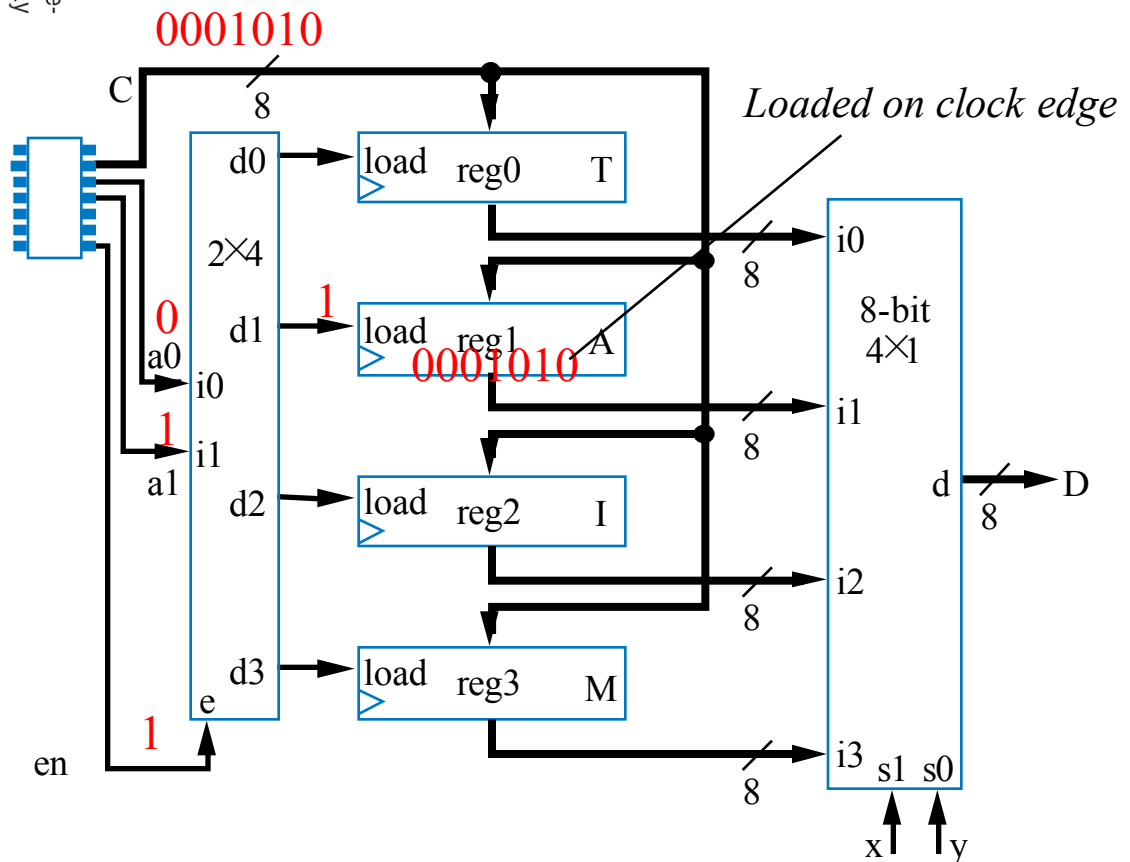- Four simultaneous values from car's computer: Temperature, Average mpg, Instantaneous mpg, Millage remaining
- To reduce wires: Computer writes only 1 value at a time, loads into one of four registers




Register Files

 - ***MxN register file*** provides efficient access to M N-bit-wide registers
 - If we have many registers but only need access one or two at a time, a register file is more efficient
 - Ex: Above mirror display (earlier example), but this time having 16 32-bit registers
 - Too many wires, and big mux is too slow



Register File

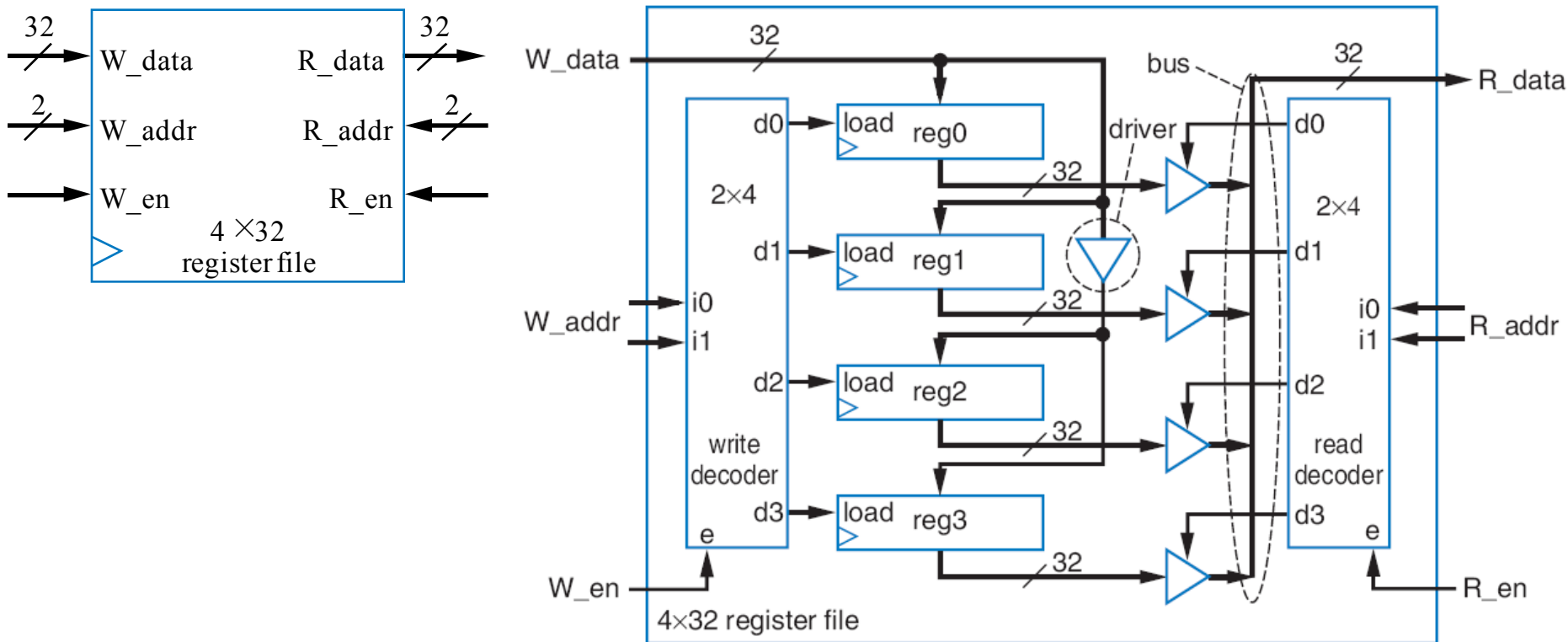- Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read





Verilog Modeling of Clocked Register File

```
module memory (R_data, W_data, W_addr, R_addr, W_en, R_en, clock);  
    parameter width = 32;  
    parameter addr_width = 2;  
    parameter number = 2**addr_width;  
  
    output [width-1:0]      R_data;  
    input  [width-1:0]      W_data;  
    input  [addr_width-1:0] W_addr, R_addr;  
    input                                W_en, R_en, clock;  
  
    reg [width-1:0] R_data;  
    reg [width-1:0] memory [number-1:0];  
  
    always @(posedge clock) begin  
        R_data = 'bz;  
        if (W_en)      memory[W_addr] = W_data;  
        else if (R_en) R_data = memory[R_addr]; //R_data will be register  
    end  
endmodule
```


Register File Timing Diagram

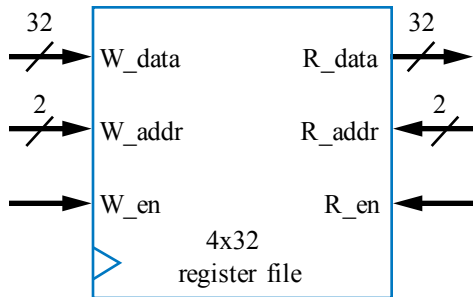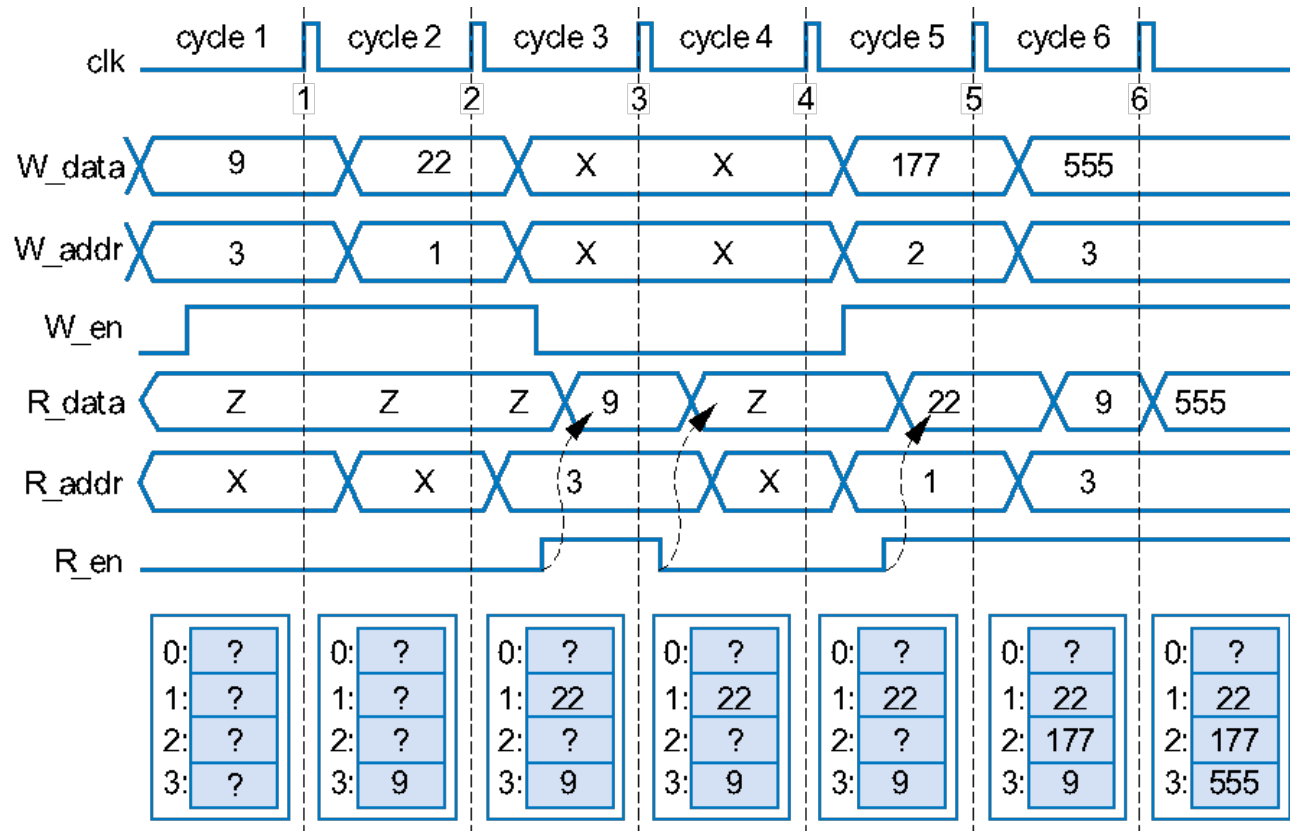- May be designed to write one register and read one register in one clock cycle
 - May be same register




Register-File Example: Above-Mirror Display

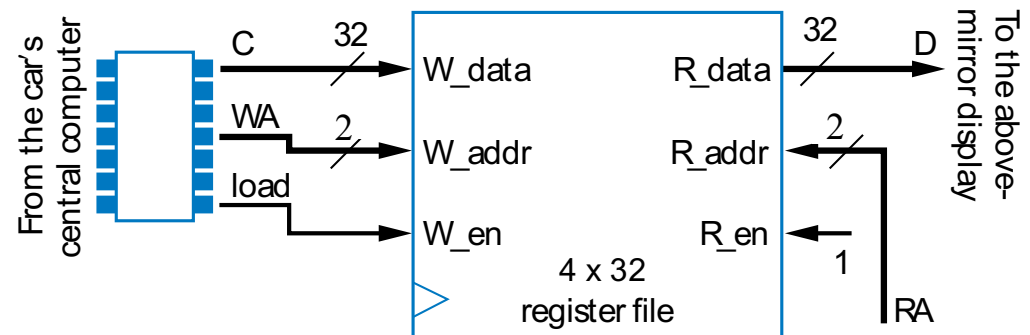- Four 32-bit registers that can be written by car's computer, and displayed
 - Use 4x32 register file
 - Simple, elegant design
- Register file hides complexity internally
 - And because only one register needs to be written and/or read at a time, internal design is simple




Shift Register

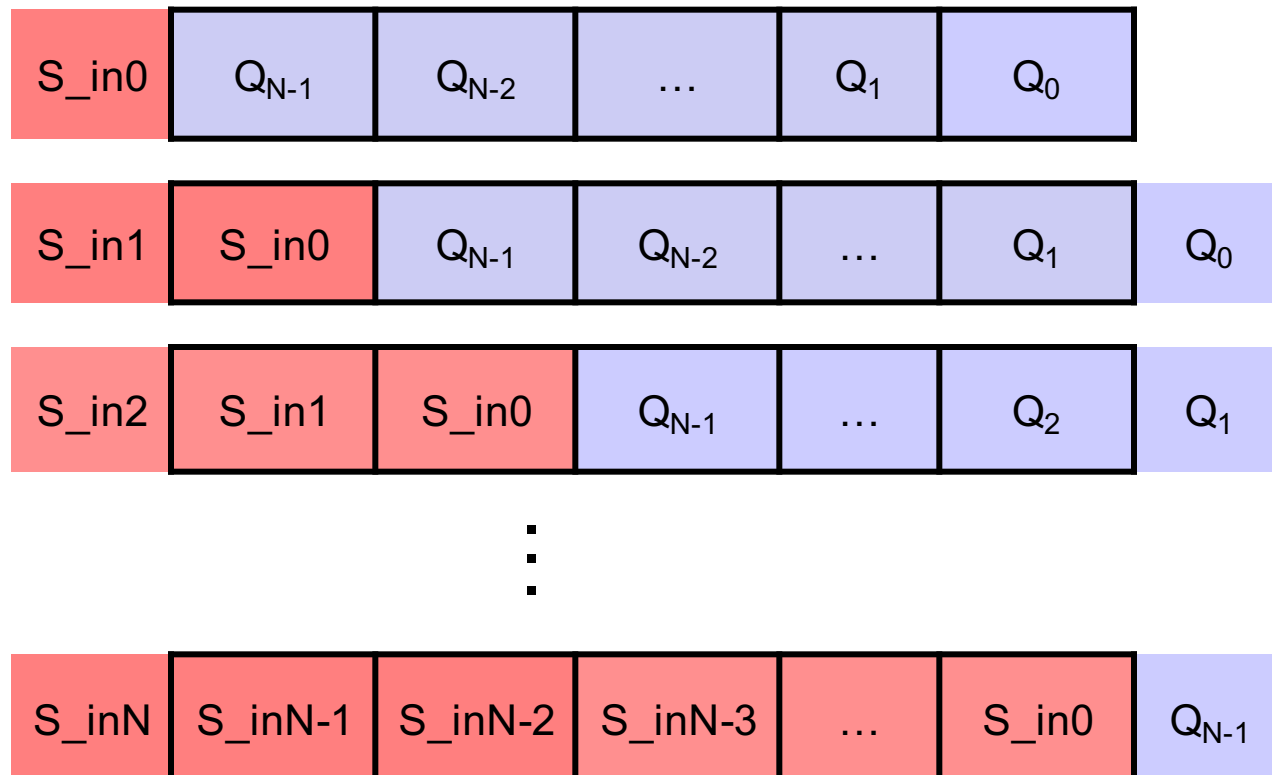- One type of register
 - Stores binary data
 - Stored data can be shifted right (MSB >> LSM) or left (MSB << LSB)
 - Example: Shift right per clock edge



Shift Register

 - Implementation:
 - Connect Q output of one flip flop to the D input of the next flip flop
 - 4-bit shift register



	IN	OUT(3:0)
Initial value:	0	0110
rising edge:	0	0011
rising edge:	0	0001
rising edge:	0	0000
rising edge:	1	1000
rising edge:	0	0100

Verilog Modeling of Shift Registers

```
module Shift_Reg (Q, Dout, Din, clock);  
    input clock, Din;  
    output Dout;  
    output [3:0] Q;  
  
    reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3]    <= Din;  
    end  
  
    assign Dout = Q[0];  
endmodule
```

Verilog Testbench for Shift Registers

```
module Test_Banch;
    parameter half_period = 50;
    wire [3:0] Q;  wire Dout;  reg  Din, clock;

    Shift_Reg UUT (Q, Dout, Din, clock);

    initial begin
        $display("*****");
        $display("The textual simulation results:");
        $display("*****");
        $monitor($time, "clock = %d  Din = %b  Q = %b  Dout = %d",
                clock, Din, Q, Dout);
    end

    initial begin
        #0    clock = 0; Din = 0;
        #300 Din = 1;
        #400 Din = 0;
    end

    always #half_period clock = ~clock;

    initial #1000 $stop;
endmodule
```


Textural Simulation Result

The textual simulation results:

0	clock = 0	Din = 0	Q = xxxx	Dout = x
50	clock = 1	Din = 0	Q = 0xxx	Dout = x
100	clock = 0	Din = 0	Q = 0xxx	Dout = x
150	clock = 1	Din = 0	Q = 00xx	Dout = x
200	clock = 0	Din = 0	Q = 00xx	Dout = x
250	clock = 1	Din = 0	Q = 000x	Dout = x
300	clock = 0	Din = 1	Q = 000x	Dout = x
350	clock = 1	Din = 1	Q = 1000	Dout = 0
400	clock = 0	Din = 1	Q = 1000	Dout = 0
450	clock = 1	Din = 1	Q = 1100	Dout = 0
500	clock = 0	Din = 1	Q = 1100	Dout = 0
550	clock = 1	Din = 1	Q = 1110	Dout = 0
600	clock = 0	Din = 1	Q = 1110	Dout = 0
650	clock = 1	Din = 1	Q = 1111	Dout = 1
700	clock = 0	Din = 0	Q = 1111	Dout = 1
750	clock = 1	Din = 0	Q = 0111	Dout = 1
800	clock = 0	Din = 0	Q = 0111	Dout = 1
850	clock = 1	Din = 0	Q = 0011	Dout = 1
900	clock = 0	Din = 0	Q = 0011	Dout = 1
950	clock = 1	Din = 0	Q = 0001	Dout = 1


Stopped at time : 1.000 ps : File "C:/Users/gzheng/test/tb.v" Line 29

Graphical Simulation Results

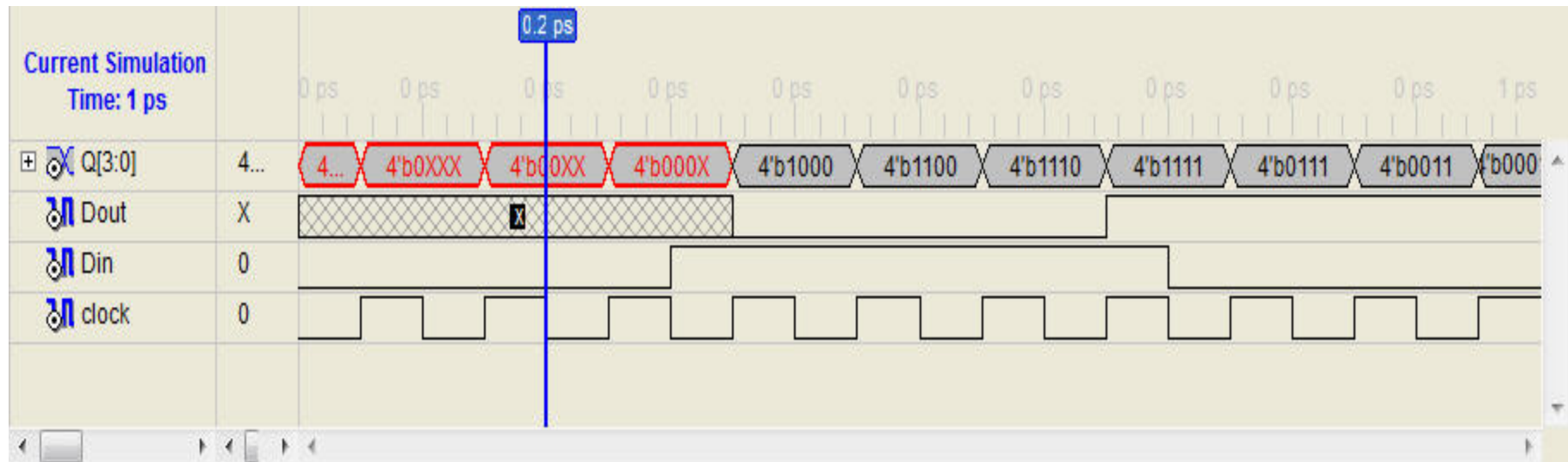

Rotate Register

 - Implementation:
 - Connect Q output of one flip flop to the D input of the next flip flop
 - Connect Q output of the last flip flop to the D input of the first flip flop
 - 4-bit rotate register



	OUT(3:0)
Initial value:	0110
rising edge:	0011
rising edge:	1001
rising edge:	1100
rising edge:	0110
rising edge:	0011

Verilog Modeling of Rotate Registers


```
module Barral_Shift_Reg (Q, clock);  
    input clock;  
    output [3:0] Q;  
  
    reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3] <= Q[0];  
    end  
  
endmodule
```

Modified Rotate Registers

```
module Barral_Shift_Reg (Q, Din, clock, ld);  
  input clock, ld, Din;  
  output [3:0] Q;  
  
  reg [3:0] Q;  
  
  always @ (posedge clock)  
  begin  
    Q[2:0] <= Q[3:1];  
    if (ld) Q[3] <= Din;  
    else    Q[3] <= Q[0];  
  end  
  
endmodule
```



Shift/Rotate Register with Control Input

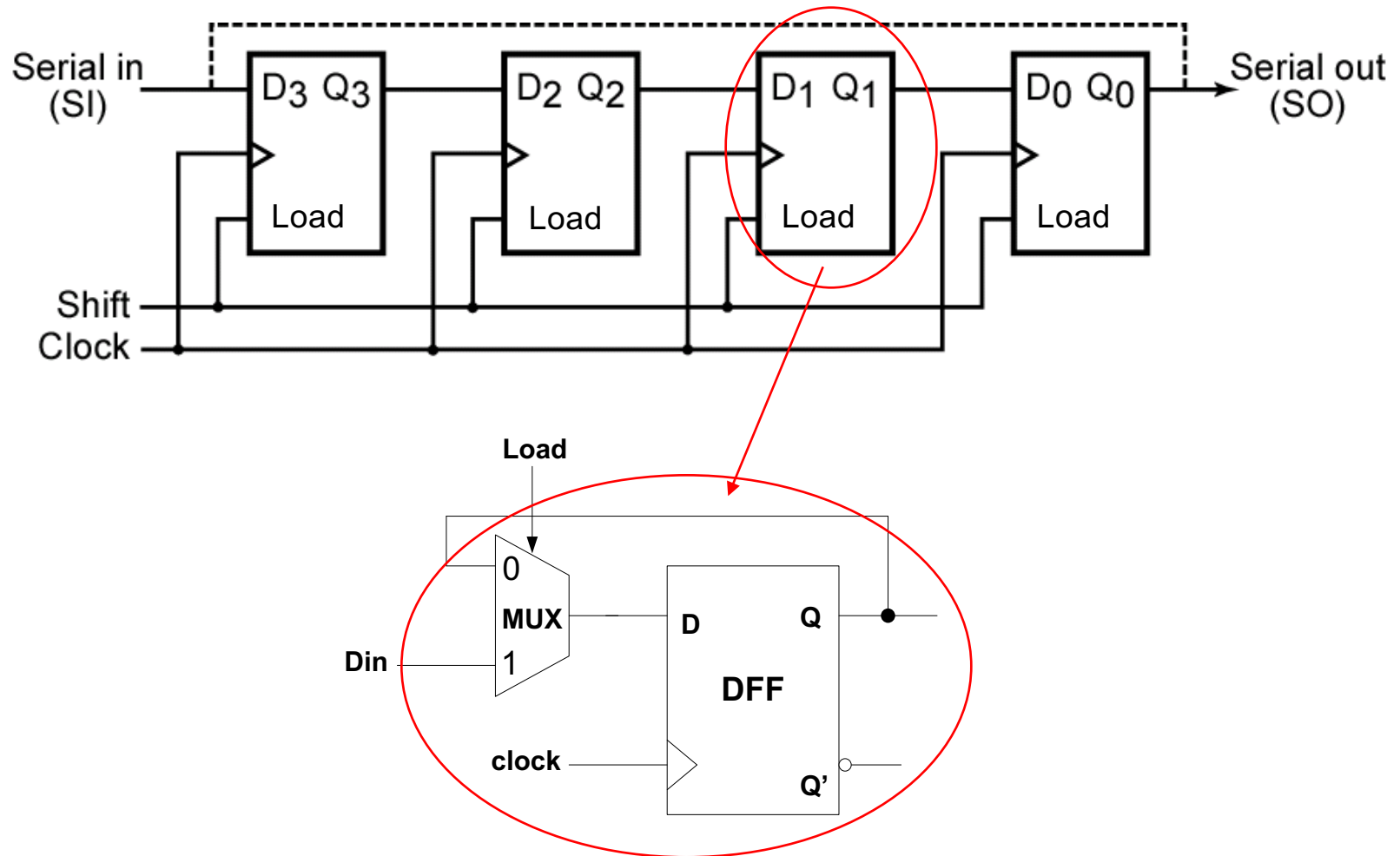 - Parallel Load control input may be used to hold the shifting



Universal Shift Register

- Multi-functional shift register





- Functions
 - the 4th input of MUX can be used for something else


Inputs		Action
Sh (Shift)	L (Load)	
0	0	no change
0	1	load
1	X	Shift Right

Shift Register Example: Above-Mirror Display

  
- Earlier example: $8 + 2 + 1 = 11$ wires from computer to registers
- Use shift registers
 - Wires: $1 + 2 + 1 = 4$
 - Computer sends one value at a time, one bit per clock cycle



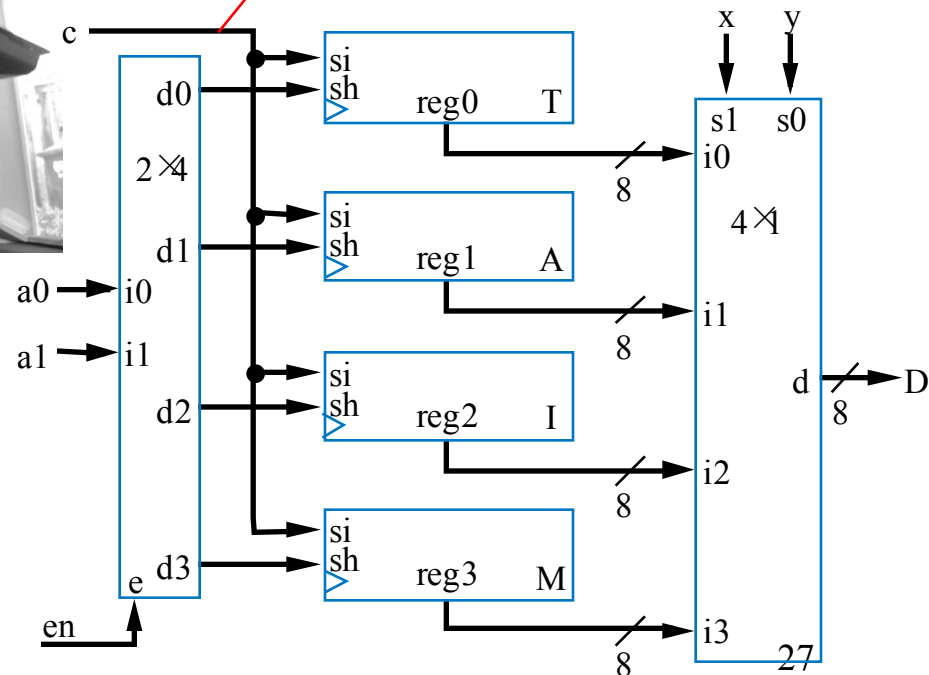Note: this line is 1 bit, rather than 8 bits like before




Application: UART Transmitter

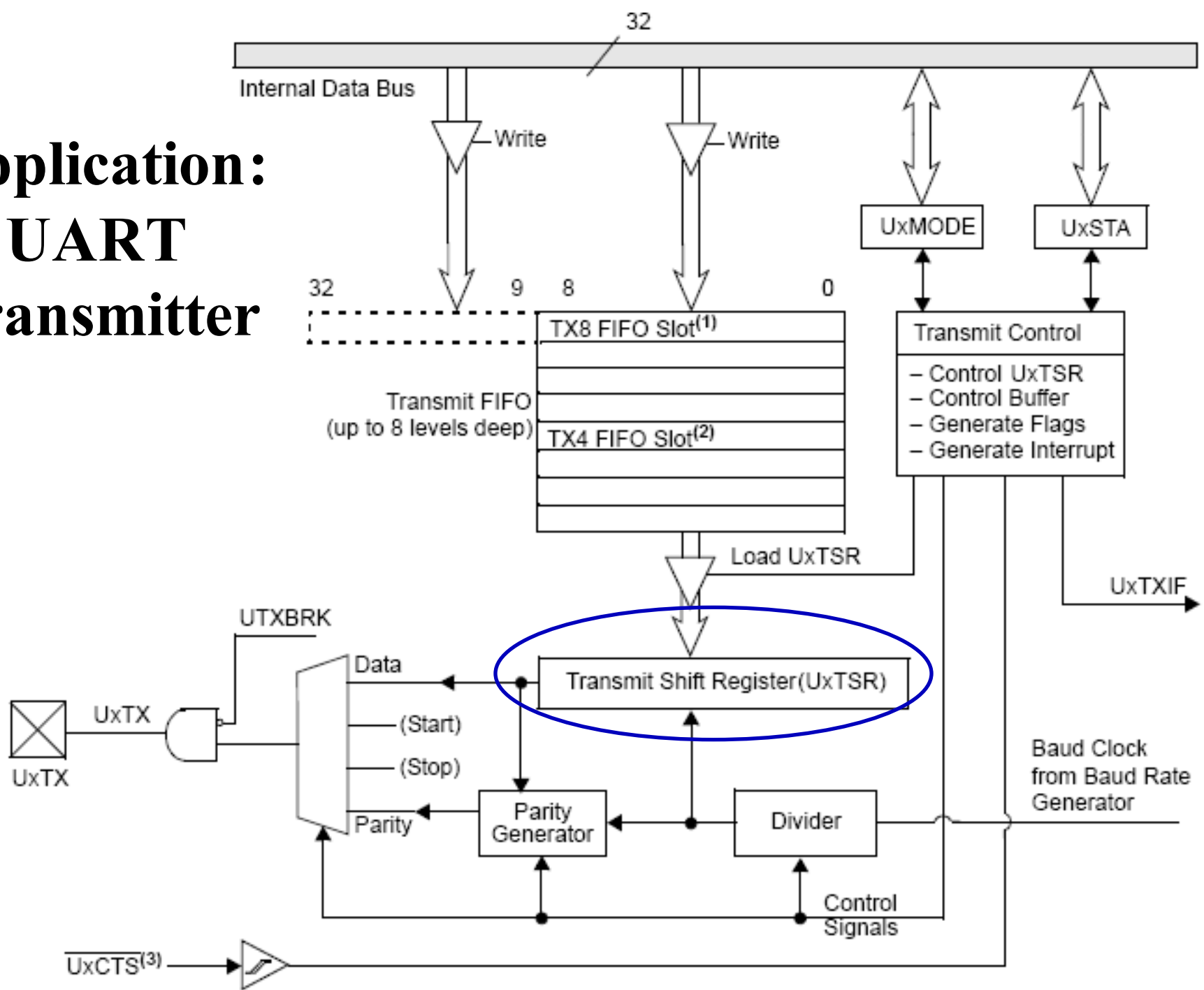

Shifters (Not Shift Register)

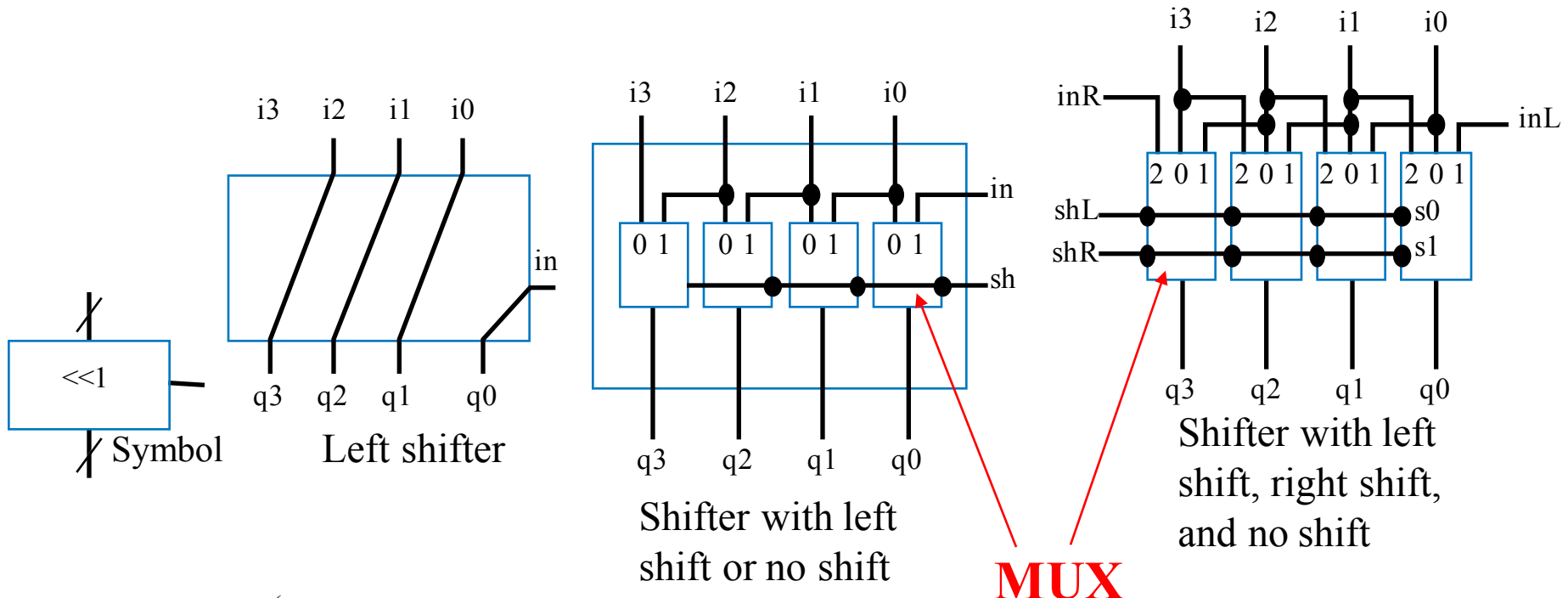- Combinational Datapath component
- Shifting (e.g., left shifting 0011 yields 0110) useful for:
 - Manipulating bits
 - Shift left once is same as multiplying by 2 (0011 (3) becomes 0110 (6))
 - Shift right once same as dividing by 2



Verilog Modeling of Shifter

```
module Shifter_0_or_1 (Q, I, in, sh);
    parameter size = 4;
    input in, sh;
    input [size-1:0] I;
    output [size-1:0] Q;


    reg [size-1:0] Q;

    always @ (sh, in, I)
    begin
        if (sh) begin Q[size-1:1] = I[size-2:0];
                    Q[0]          = in;
                end
        else Q = I;
    end

endmodule
```


Shifter Example: Approximate Celsius to Fahrenheit Converter

 - Convert 8-bit Celsius input to 8-bit Fahrenheit output
 - $F = C * 9/5 + 32$
 - Approximate: $F = C * 2 + 32$
 - Use left shift: $F = \text{left_shift}(C) + 32$



Shifter Example: Temperature Averager

 - Four registers storing a history of temperatures
- Want to output the average of those temperatures
- Add, then divide by four
 - Same as shift right by 2
 - Use three adders, and right shift by two



Bigger Shifter

- A shifter that can shift by any amount
 - But shifting too many bits in one shifter could require design with too many wires
- More elegant design
 - Chain shifters
 - E.g.: Can achieve any shift of 0..7 bits by enabling the correct combination of 4, 2, 1 bit shifters

